



## *GATE PREVIOUS YEAR SOLVED PAPERS*

### **Electronics & Telecommunications Previous Year Solved Papers**

**GATEFORUM** Pioneers in Digital courses for GATE since 2008 has long history of training students through innovative courses. Currently GATEFORUM offers a wide range of courses from eGATE, GATE Online, Gdrive to Online TarGATE. Since inception, we have trained more 3,00,000 students since inception.

**For more details visit [gateforumonline.com](http://gateforumonline.com)**

**GENERAL APTITUDE****Q. No. 1 to 5 Carry One Mark Each**

1. Choose the grammatically CORRECT sentence:

- (A) Two and two add four                      (B) Two and two become four  
(C) Two and two are four                      (D) Two and two make four

**Answer: (D)**

---

2. Statement: You can always give me a ring whenever you need.

Which one of the following is the best inference from the above statement?

- (A) Because I have a nice caller tune  
(B) Because I have a better telephone facility  
(C) Because a friend in need is a friend indeed  
(D) Because you need not pay towards the telephone bills when you give me a ring

**Answer: (C)**

---

3. In the summer of 2012, in New Delhi, the mean temperature of Monday to Wednesday was 41°C and of Tuesday to Thursday was 43°C. If the temperature on Thursday was 15% higher than that of Monday, then the temperature in °C on Thursday was

- (A) 40                      (B) 43                      (C) 46                      (D) 49

**Answer: (C)**

---

4. Complete the sentence:

Dare \_\_\_\_\_ mistakes.

- (A) commit                      (B) to commit                      (C) committed                      (D) committing

**Answer: (B)**

---

5. They were requested not to quarrel with others.

Which one of the following options is the closest in meaning to the word quarrel?

- (A) make out                      (B) call out                      (C) dig out                      (D) fall out

**Answer: (D)**

**Q. No. 6 – 10 Carry Two Marks Each**

6. A car travels 8 km in the first quarter of an hour, 6 km in the second quarter and 16km in the third quarter. The average speed of the car in km per hour over the entire journey is

(A) 30 (B) 36 (C) 40 (D) 24

**Answer: (C)**

7. Find the sum to n terms of the series  $10 + 84 + 734 + \dots$

(A)  $\frac{9(9^n + 1)}{10} + 1$  (B)  $\frac{9(9^n - 1)}{8} + 1$  (C)  $\frac{9(9^n - 1)}{8} + n$  (D)  $\frac{9(9^n - 1)}{8} + n^2$

**Answer: (D)**

8. Statement: There were different streams of freedom movements in colonial India carried out by the moderates, liberals, radicals, socialists, and so on.

Which one of the following is the best inference from the above statement?

- (A) The emergence of nationalism in colonial India led to our Independence  
(B) Nationalism in India emerged in the context of colonialism  
(C) Nationalism in India is homogeneous  
(D) Nationalism in India is heterogeneous

**Answer: (D)**

9. The set of values of p for which the roots of the equation  $3x^2 + 2x + p(p - 1) = 0$  are of opposite sign is

(A)  $(-\infty, 0)$  (B)  $(0, 1)$  (C)  $(1, \infty)$  (D)  $(0, \infty)$

**Answer: (B)**

10. What is the chance that a leap year, selected at random, will contain 53 Sundays?

(A)  $2/7$  (B)  $3/7$  (C)  $1/7$  (D)  $5/7$

**Answer: (A)**

**ELECTRONICS AND COMMUNICATIONS****Q. No. 1 – 25 Carry One Mark Each**

1. A bulb in a staircase has two switches, one switch being at the ground floor and the other one at the first floor. The bulb can be turned ON and also can be turned OFF by any one of the switches irrespective of the state of the other switch. The logic of switching of the bulb resembles
- (A) an AND gate (B) an OR gate  
(C) an XOR gate (D) a NAND gate

**Answer: (C)**

---

2. Consider a vector field  $\vec{A}(\vec{r})$ . The closed loop line integral  $\oint \vec{A} \cdot d\vec{l}$  can be expressed as
- (A)  $\oint (\nabla \times \vec{A}) \cdot d\vec{s}$  over the closed surface bounded by the loop  
(B)  $\oint (\nabla \cdot \vec{A}) dv$  over the closed volume bounded by the loop  
(C)  $\oint (\nabla \cdot \vec{A}) dv$  over the open volume bounded by the loop  
(D)  $\oint (\nabla \times \vec{A}) \cdot d\vec{s}$  over the closed surface bounded by the loop

**Answer: (D)**

---

3. Two systems with impulse responses  $h_1(t)$  and  $h_2(t)$  are connected in cascade. Then the overall impulse response of the cascaded system is given by
- (A) Product of  $h_1(t)$  and  $h_2(t)$  (B) Sum of  $\frac{1}{4}$  and  $\frac{1}{9}$   
(C) Convolution of  $\frac{1}{4}$  and  $\frac{1}{9}$  (D) Subtraction of  $h_2(t)$  from  $h_1(t)$

**Answer: (C)**

---

4. In a forward biased p-n junction diode, the sequence of events that best describes the mechanism of current flow is
- (A) injection, and subsequent diffusion and recombination of minority carriers  
(B) injection, and subsequent drift and generation of minority carriers

- (C) extraction, and subsequent diffusion and generation of minority carriers
- (D) extraction, and subsequent drift and recombination of minority carriers

**Answer: (A)**

---

5. In IC technology, dry oxidation (using dry oxygen) as compared to wet oxidation (using steam or water vapor) produces
- (A) superior quality oxide with a higher growth rate
  - (B) inferior quality oxide with a higher growth rate
  - (C) inferior quality oxide with a lower growth rate
  - (D) superior quality oxide with a lower growth rate

**Answer: (B)**

---

6. The maximum value of  $\theta$  until which the approximation  $\theta \approx \sin \theta$  holds to within 10% error is
- (A)  $10^\circ$
  - (B)  $18^\circ$
  - (C)  $50^\circ$
  - (D)  $90^\circ$

**Answer: (B)**

---

7. The divergence of the vector field  $\vec{A} = x\hat{a}_x + y\hat{a}_y + z\hat{a}_z$  is
- (A) 0
  - (B)  $1/3$
  - (C) 1
  - (D) 3


**Answer: (D)**

---

8. The impulse response of a system is  $h(t) = t u(t)$ . For an input  $u(t-1)$ , the output is
- (A)  $\frac{t^2}{2} u(t)$
  - (B)  $\frac{t(t-1)}{2} u(t-1)$
  - (C)  $\frac{(t-1)^2}{2} u(t-1)$
  - (D)  $\frac{t^2-1}{2} u(t-1)$

**Answer: (C)**

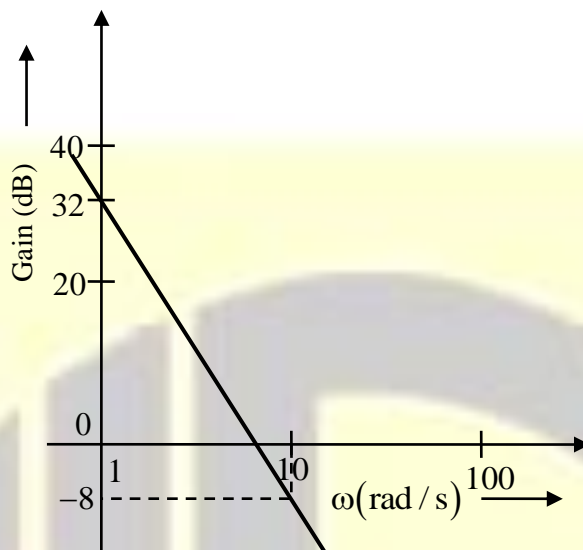9. The Bode plot of a transfer function  $G(s)$  is shown in the figure below




The gain  $(20 \log |G(s)|)$  is 32 dB and -8 dB at 1 rad/s and 10 rad/s respectively. The phase is negative for all  $\omega$ . The  $G(s)$  is

- (A)  $\frac{39.8}{s}$       (B)  $\frac{39.8}{s^2}$       (C)  $\frac{32}{s}$       (D)  $\frac{32}{s^2}$

**Answer: (B)**

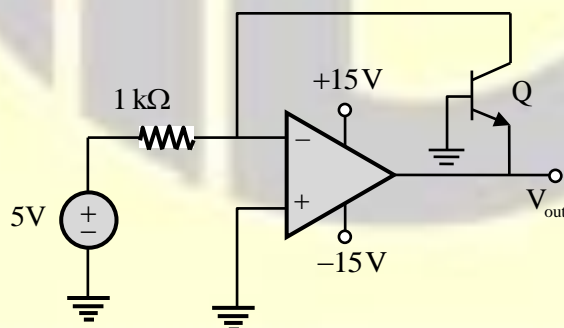10. In the circuit shown below what is the output voltage ( $V_{out}$ ) if a silicon transistor Q and an ideal op-amp are used?




- (A) -15V      (B) -0.7V      (C) +0.7V      (D) +15V

**Answer: (A)**



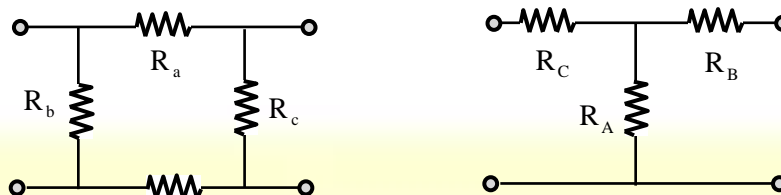11. Consider a delta connection of resistors and its equivalent star connection as shown below.



If all elements of the delta connection are scaled by a factor  $k$ ,  $k > 0$ , the elements of the corresponding star equivalent will be scaled by a factor of

- (A)  $k^2$                       (B)  $k$                       (C)  $1/k$                       (D)  $\sqrt{k}$

**Answer: (B)**

12. For 8085 microprocessor, the following program is executed

```
MVI A, 05H;
MVI B, 05H;
PTR:  ADD B;
      DCR B;
      JNZ PTR;
      ADI 03h;
      HLT;
```

At the end of program, accumulator contains

- (A) 17 H                      (B) 20 H                      (C) 23 H                      (D) 05 H

**Answer: (A)**

13. The bit rate of a digital communication system is  $R$  kbits/s. The modulation used is 32-QAM. The minimum bandwidth required for ISI free transmission is

- (A)  $R/10$  Hz                      (B)  $R/10$  kHz                      (C)  $R/5$  Hz                      (D)  $R/5$  kHz


**Answer: (C)**

14. For a periodic signal  $v(t) = 30\sin 100t + 10\cos 300t + 6\sin(500t + \pi/4)$ , the fundamental frequency in rad/s

- (A) 100                      (B) 300                      (C) 500                      (D) 1500

**Answer: (A)**

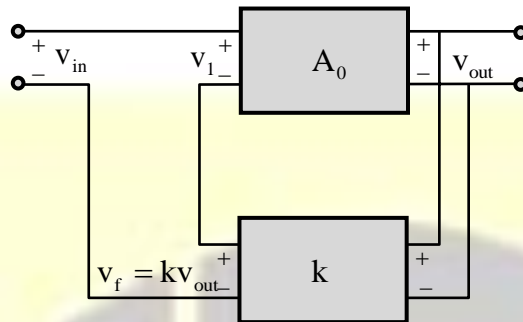15. In a voltage-voltage feedback as shown below, which one of the following statements is TRUE if the gain  $k$  is increased?



- (A) The input impedance increases and output impedance decreases
- (B) The input impedance increases and output impedance also increases
- (C) The input impedance decreases and output impedance also decreases
- (D) The input impedance decreases and output impedance increases

**Answer: (A)**

16. A band-limited signal with a maximum frequency of 5 kHz is to be sampled. According to the sampling theorem, the sampling frequency which is not valid is
- (A) 5 kHz                      (B) 12 kHz                      (C) 15 kHz                      (D) 20 kHz

**Answer: (A)**

17. In a MOSFET operating in the saturation region, the channel length modulation effect causes
- (A) an increase in the gate-source capacitance
  - (B) a decrease in the Transconductance
  - (C) a decrease in the unity-gain cutoff frequency
  - (D) a decrease in the output resistance

**Answer: (D)**

18. Which one of the following statements is NOT TRUE for a continuous time causal and stable LTI system?
- (A) All the poles of the system must lie on the left side of the  $j\omega$  axis
  - (B) Zeros of the system can lie anywhere in the  $s$ -plane



- (C) All the poles must lie within  $|s| = 1$
- (D) All the roots of the characteristic equation must be located on the left side of the  $j\omega$  axis

**Answer: (B)**

19. The minimum Eigen value of the following matrix is

$$\begin{bmatrix} 3 & 5 & 2 \\ 5 & 12 & 7 \\ 2 & 7 & 5 \end{bmatrix}$$

- (A) 0                      (B) 1                      (C) 2                      (D) 3


**Answer: (A)**

20. A polynomial  $f(x) = a_4x^4 + a_3x^3 + a_2x^2 + a_1x - a_0$  with all coefficients positive has

- (A) no real roots
- (B) no negative real root
- (C) odd number of real roots
- (D) at least one positive and one negative real root

**Answer: (D)**

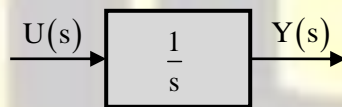
21. Assuming zero initial condition, the response  $y(t)$  of the system given below to a unit step input  $u(t)$  is



- (A)  $u(t)$                       (B)  $tu(t)$                       (C)  $\frac{t^2}{2}u(t)$                       (D)  $e^{-t}u(t)$

**Answer: (D)**

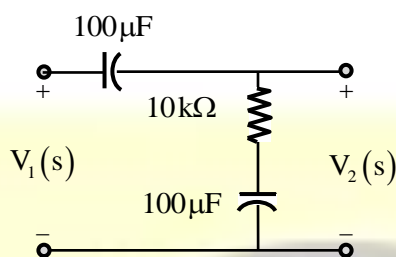22. The transfer function  $\frac{V_2(s)}{V_1(s)}$  of the circuit shown below is



- (A)  $\frac{0.5s+1}{s+1}$  (B)  $\frac{3s+6}{s+2}$  (C)  $\frac{s+2}{s+1}$  (D)  $\frac{s+1}{s+2}$

**Answer: (D)**

23. A source  $v_s(t) = V \cos 100\pi t$  has an internal impedance of  $(4 + j3)\Omega$ . If a purely resistive load connected to this source has to extract the maximum power out of the source, its value in  $\Omega$  should be
- (A) 3 (B) 4 (C) 5 (D) 7

**Answer: (C)**

24. The return loss of a device is found to be 20 dB. The voltage standing wave ratio (VSWR) and magnitude of reflection coefficient are respectively
- (A) 1.22 and 0.1 (B) 0.81 and 0.1 (C) -1.22 and 0.1 (D) 2.44 and 0.2

**Answer: (A)**

25. Let  $g(t) = e^{-\pi t^2}$ , and  $h(t)$  is a filter matched to  $g(t)$ . If  $g(t)$  is applied as input to  $h(t)$ , then the Fourier transform of the output is
- (A)  $e^{-\pi f^2}$  (B)  $e^{-\pi f^2/2}$  (C)  $e^{-\pi|f|}$  (D)  $e^{-2\pi f^2}$

**Answer: (D)**

Q. No. 26 – 55 Carry Two Marks Each

26. Let  $U$  and  $V$  be two independent zero mean Gaussian random variables of variances  $\frac{1}{4}$  and  $\frac{1}{9}$  respectively. The probability  $P(3V \geq 2U)$  is
- (A)  $4/9$                       (B)  $1/2$                       (C)  $2/3$                       (D)  $5/9$

**Answer: (B)**


27. Let  $A$  be an  $m \times n$  matrix and  $B$  an  $n \times m$  matrix. It is given that determinant  $(I_m + AB) = \text{determinant}(I_n + BA)$ , where  $I_k$  is the  $k \times k$  identity matrix. Using the above property, the determinant of the matrix given below is

$$\begin{bmatrix} 2 & 1 & 1 & 1 \\ 1 & 2 & 1 & 1 \\ 1 & 1 & 2 & 1 \\ 1 & 1 & 1 & 2 \end{bmatrix}$$

- (A) 2                      (B) 5                      (C) 8                      (D) 16

**Answer: (B)**

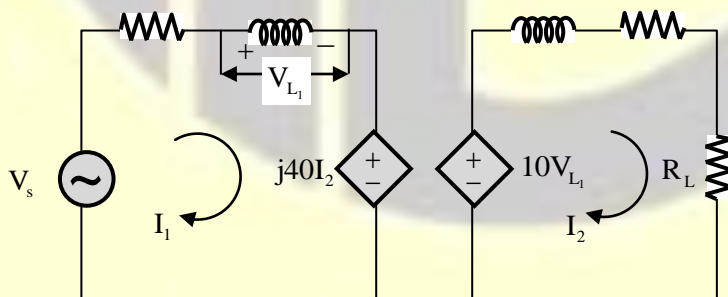28. In the circuit shown below, if the source voltage  $V_s = 100 \angle 53.13^\circ \text{V}$  then the Thevenin's equivalent voltage in Volts as seen by the load resistance  $R_L$  is



- (A)  $100 \angle 90^\circ$                       (B)  $800 \angle 0^\circ$                       (C)  $800 \angle 90^\circ$                       (D)  $100 \angle 60^\circ$

**Answer: (C)**



## *GATE REFRESHER COURSE*


Electronics & Telecommunications Engineering

**GATEFORUM** Pioneers in Digital courses for GATE since 2008 offers **GATE refresher course** giving you access to video solutions for previous 11 years GATE questions and Topic-wise formula Compendium (Handbook).

**Enroll now and get 20% discount use  
Promo Code **GATEPAPERS****

**For more details visit [gateforumonline.com](http://gateforumonline.com)**

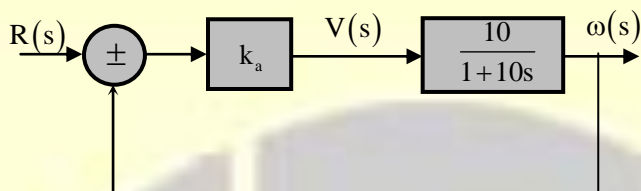
29. The open-loop transfer function of a dc motor is given as  $\frac{\omega(s)}{V_a(s)} = \frac{10}{1+10s}$ , when connected in feedback as shown below, the approximate value of  $k_a$  that will reduce the time constant of the closed loop system by one hundred times as compared to that of the open-loop system is



- (A) 1                      (B) 5                      (C) 10                      (D) 100

**Answer: (C)**

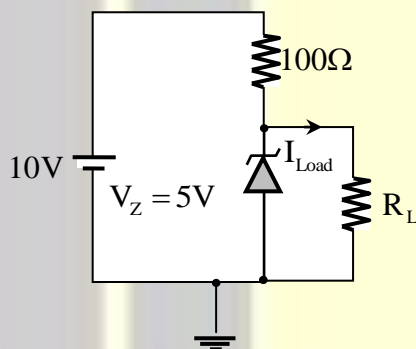
30. In the circuit shown below, the knee current of the ideal Zener diode is 10mA. To maintain 5V across  $R_L$ , the minimum value of  $R_L$  in  $\Omega$  and the minimum power rating of the Zener diode in mW, respectively, are



- (A) 125 and 125                      (B) 125 and 250  
(C) 250 and 125                      (D) 250 and 250

**Answer: (B)**

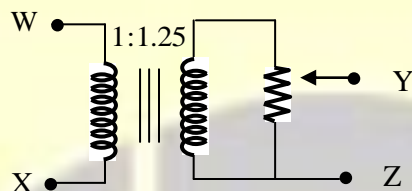31. The following arrangement consists of an ideal transformer and an attenuator which attenuates by a factor of 0.8. An ac voltage  $V_{WX1} = 100V$  is applied across WX to get an open circuit voltage  $V_{YZ1}$  across YZ. Next, an ac voltage  $V_{YZ2} = 100V$  is applied across YZ to get an open circuit voltage  $V_{WX2}$  across WX. Then,  $V_{YZ1} / V_{WX1}$ ,  $V_{WX2} / V_{YZ2}$  are respectively.



- (A) 125/100 and 80/100  
(B) 100/100 and 80/100  
(C) 100/100 and 100/100  
(D) 80/100 and 80/100

**Answer: (B)**

32. Two magnetically uncoupled inductive coils have Q factors  $q_1$  and  $q_2$  at the chosen operating frequency. Their respective resistances are  $R_1$  and  $R_2$ . When connected in series, their effective Q factor at the same operating frequency is

- (A)  $q_1 + q_2$   
(B)  $\left(\frac{1}{q_1}\right) + \left(\frac{1}{q_2}\right)$   
(C)  $\frac{(q_1 R_1 + q_2 R_2)}{(R_1 + R_2)}$   
(D)  $\frac{(q_1 R_2 + q_2 R_1)}{(R_1 + R_2)}$

**Answer: (C)**


33. The impulse response of a continuous time system is given by  $h(t) = \delta(t-1) + \delta(t-3)$ . The value of the step response at  $t = 2$  is

- (A) 0  
(B) 1  
(C) 2  
(D) 3

**Answer: (B)**



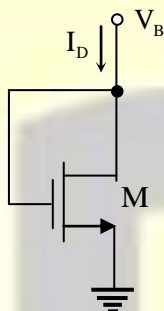
34. The small-signal resistance (i.e.,  $\frac{dV_B}{dI_D}$ ) in  $k\Omega$  offered by the n-channel MOSFET M shown in the figure below, at a bias point of  $V_B = 2V$  is (device data for M: device Transconductance parameter  $k_N = \mu_n C_{ox} (W/L) = 40\mu A/V^2$ , threshold voltage  $V_{TN} = 1V$ , and neglect body effect and channel length modulation effects)



- (A) 12.5                      (B) 25                      (C) 50                      (D) 100

**Answer: (B)**

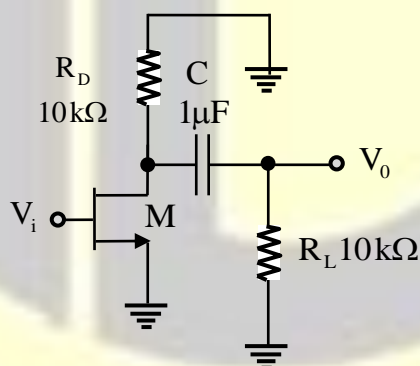35. The ac schematic of an NMOS common-source stage is shown in the figure below, where part of the biasing circuits has been omitted for simplicity. For the n-channel MOSFET M, the Transconductance  $g_m = 1mA/V$ , and body effect and channel length modulation effect are to be neglected. The lower cutoff frequency in Hz of the circuit is approximately at



- (A) 8                      (B) 32                      (C) 50                      (D) 200

**Answer: (A)**

36. A system is described by the differential equation  $\frac{d^2y}{dt^2} + 5\frac{dy}{dt} + 6y(t) = x(t)$ .

Let  $x(t)$  be a rectangular pulse given by

$$x(t) = \begin{cases} 1 & 0 < t < 2 \\ 0 & \text{otherwise} \end{cases}$$

Assuming that  $y(0)=0$  and  $\frac{dy}{dt} = 0$  at  $t = 0$ , the Laplace transform of  $y(t)$  is

- (A)  $\frac{e^{-2s}}{s(s+2)(s+3)}$  (B)  $\frac{1-e^{-2s}}{s(s+2)(s+3)}$   
(C)  $\frac{e^{-2s}}{(s+2)(s+3)}$  (D)  $\frac{1-e^{-2s}}{(s+2)(s+3)}$

**Answer: (B)**

---

37. A system described by a linear, constant coefficient, ordinary, first order differential equation has an exact solution given by  $y(t)$  for  $t > 0$ , when the forcing function is  $x(t)$  and the initial condition is  $y(0)$ . If one wishes to modify the system so that the solution becomes  $-2y(t)$  for  $t > 0$ , we need to

- (A) change the initial condition to  $-y(0)$  and the forcing function to  $2x(t)$   
(B) change the initial condition to  $2y(0)$  and the forcing function to  $-x(t)$   
(C) change the initial condition to  $j\sqrt{2}y(0)$  and the forcing function to  $j\sqrt{2}x(t)$   
(D) change the initial condition to  $-2y(0)$  and the forcing function to  $-2x(t)$

**Answer: (D)**

---

38. Consider two identically distributed zero-mean random variables  $U$  and  $V$ . Let the cumulative distribution functions of  $U$  and  $2V$  be  $F(x)$  and  $G(x)$  respectively. Then, for all values of  $x$

- (A)  $F(x) - G(x) \leq 0$  (B)  $F(x) - G(x) \geq 0$   
(C)  $(F(x) - G(x)) \cdot x \leq 0$  (D)  $(F(x) - G(x)) \cdot x \geq 0$

**Answer: (D)**

39. The DFT of vector  $[a \ b \ c \ d]$  is the vector  $[\alpha \ \beta \ \gamma \ \delta]$ . Consider the product


$$[p \ q \ r \ s] = [a \ b \ c \ d] \begin{bmatrix} a & b & c & d \\ d & a & b & c \\ c & d & a & b \\ b & c & d & a \end{bmatrix}$$

The DFT of the vector  $[p \ q \ r \ s]$  is a scaled version of

- (A)  $[\alpha^2 \ \beta^2 \ \gamma^2 \ \delta^2]$  (B)  $[\sqrt{\alpha} \ \sqrt{\beta} \ \sqrt{\gamma} \ \sqrt{\delta}]$   
(C)  $[\alpha + \beta \ \beta + \delta \ \delta + \gamma \ \gamma + \alpha]$  (D)  $[\alpha \ \beta \ \gamma \ \delta]$

**Answer: (A)**

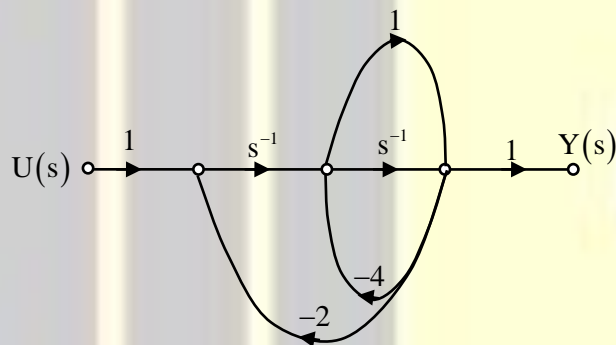
40. The signal flow graph for a system is given below. The transfer function  $\frac{Y(s)}{U(s)}$  for this system is



- (A)  $\frac{s+1}{5s^2+6s+2}$  (B)  $\frac{s+1}{s^2+6s+2}$  (C)  $\frac{s+1}{s^2+4s+2}$  (D)  $\frac{1}{5s^2+6s+2}$

**Answer: (A)**

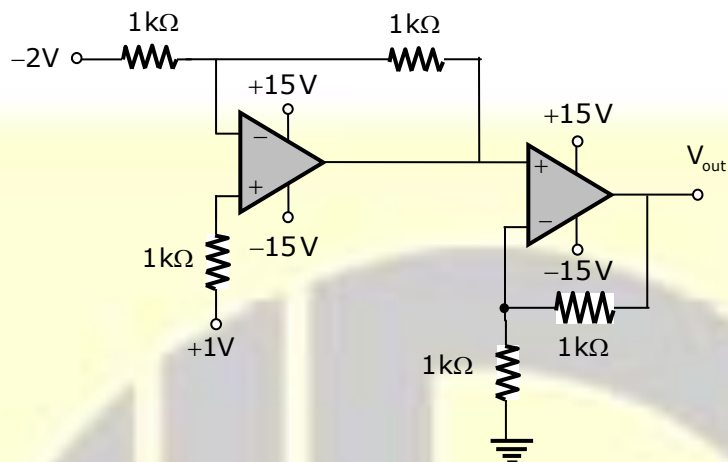
41. In the circuit shown below the op-amps are ideal. The  $V_{out}$  in Volts is



- (A) 4                      (B) 6                      (C) 8                      (D) 10

**Answer: (C)**

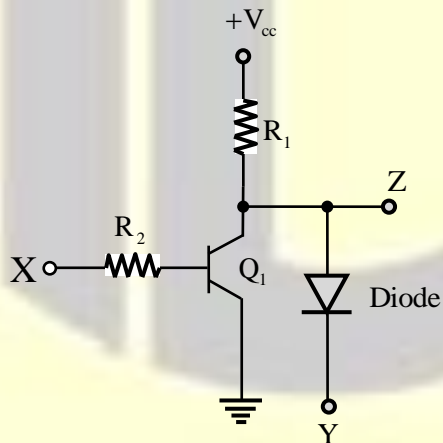
42. In the circuit shown below,  $Q_1$  has negligible collector-to-emitter saturation voltage and the diode drops negligible voltage across it under forward bias. If  $V_{cc}$  is +5V, X and Y are digital signals with 0 V as logic 0 and  $V_{cc}$  as logic 1, then the Boolean expression for Z is



- (A)  $XY$                       (B)  $\bar{X}Y$                       (C)  $X\bar{Y}$                       (D)  $\bar{X}\bar{Y}$

**Answer: (D)**

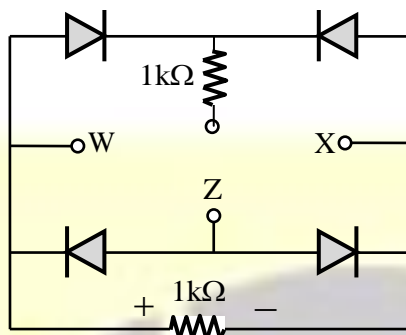
43. A voltage  $1000\sin\omega t$  Volts is applied across YZ. Assuming ideal diodes, the voltage measured across WX in Volts, is



- (A)  $\sin\omega t$  (B)  $(\sin\omega t + |\sin\omega t|)/2$   
(C)  $(\sin\omega t - |\sin\omega t|)/2$  (D) 0 for all  $t$

**Answer: (D)**

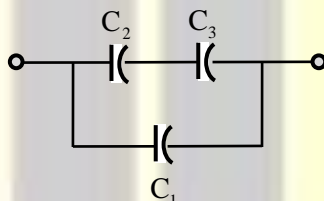44. Three capacitors  $C_1, C_2$  and  $C_3$  whose values are  $10\mu\text{F}$ ,  $5\mu\text{F}$ , and  $2\mu\text{F}$  respectively, have breakdown voltages of 10V, 5V, and 2V respectively. For the interconnection shown below, the maximum safe voltage in Volts that can be applied across the combination, and the corresponding total charge in  $\mu\text{C}$  stored in the effective capacitance across the terminals are respectively.




- (A) 2.8V and  $36\mu\text{C}$  (B) 7V and  $119\mu\text{C}$   
(C) 2.8V and  $32\mu\text{C}$  (D) 7V and  $80\mu\text{C}$

**Answer: (C)**





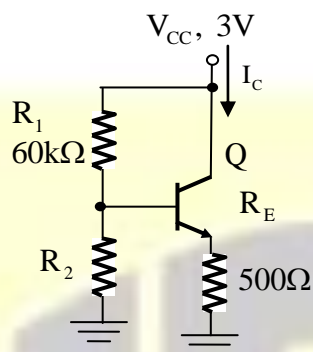46. In the circuit shown below, the silicon npn transistor Q has a very high value of  $\beta$ . The required value of  $R_2$  in  $k\Omega$  to produce  $I_C = 1\text{mA}$  is



- (A) 20                      (B) 30                      (C) 40                      (D) 50

**Answer: (D)**


47. Let  $U$  and  $V$  be two independent and identically distributed random variables such that  $P(U = +1) = P(U = -1) = \frac{1}{2}$ . The entropy  $H(U + V)$  in bits is

- (A)  $3/4$                       (B) 1                      (C)  $3/2$                       (D)  $\log_2 3$

**Answer: (C)**
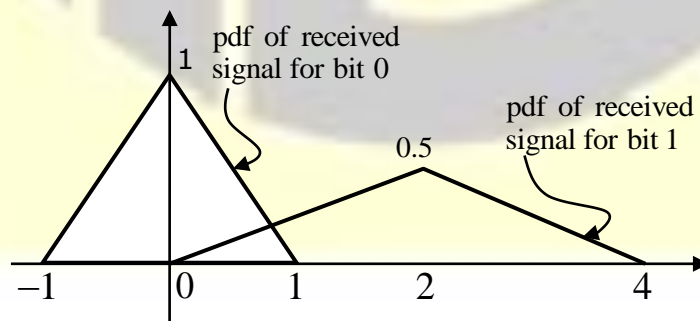
### Common Data Questions: 48 & 49

Bits 1 and 0 are transmitted with equal probability. At the receiver, the pdf of the respective received signals for both bits are as shown below.



48. If the detection threshold is 1, the BER will be

- (A)  $\frac{1}{2}$                       (B)  $\frac{1}{4}$                       (C)  $\frac{1}{8}$                       (D)  $\frac{1}{16}$

**Answer: (D)**


49. The optimum threshold to achieve minimum bit error rate (BER) is

- (A)  $\frac{1}{2}$                       (B)  $\frac{4}{5}$                       (C) 1                      (D)  $\frac{3}{2}$

**Answer: (B)**

**Common Data Questions: 50 & 51**

Consider the following figure

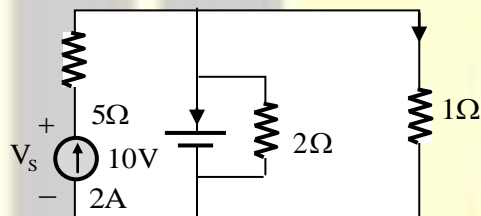

50. The current  $I_s$  in Amps in the voltage source, and voltage  $V_s$  in Volts across the current source respectively, are

- (A) 13, -20                      (B) 8, -10                      (C) -8, 20                      (D) -13, 20

**Answer: (D)**

51. The current in the  $1\Omega$  resistor in Amps is


- (A) 2                      (B) 3.33                      (C) 10                      (D) 12

**Answer: (C)**

**Linked Answer Questions: Q.52 to Q.55 Carry Two Marks Each**

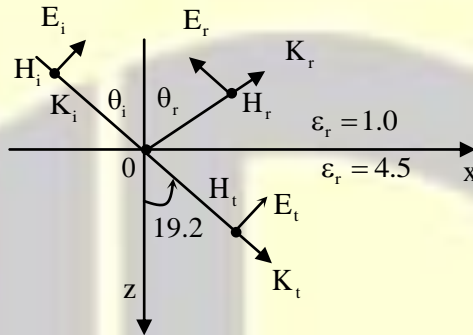**Statement for Linked Answer Questions: 52 & 53**

A monochromatic plane wave of wavelength  $\lambda = 600\mu\text{m}$  is propagating in the direction as shown in the figure below.  $\vec{E}_i$ ,  $\vec{E}_r$ , and  $\vec{E}_t$  denote incident, reflected, and transmitted electric field vectors associated with the wave.



52. The angle of incidence  $\theta_i$  and the expression for  $\vec{E}_i$  are

- (A)  $60^\circ$  and  $\frac{E_0}{\sqrt{2}}(\hat{a}_x - \hat{a}_z)e^{-j\frac{\pi \times 10^4(x+z)}{3\sqrt{2}}}$  V/m      (B)  $45^\circ$  and  $\frac{E_0}{\sqrt{2}}(\hat{a}_x + \hat{a}_z)e^{j\frac{\pi \times 10^4 z}{3}}$  V/m
- (C)  $45^\circ$  and  $\frac{E_0}{\sqrt{2}}(\hat{a}_x - \hat{a}_z)e^{-j\frac{\pi \times 10^4(x+z)}{3\sqrt{2}}}$  V/m      (D)  $65^\circ$  and  $\frac{E_0}{\sqrt{2}}(\hat{a}_x - \hat{a}_z)e^{-j\frac{\pi \times 10^4 z}{3}}$  V/m

**Answer: (4)**


53. The expression for  $\vec{E}_r$  is

- (A)  $0.23\frac{E_0}{\sqrt{2}}(\hat{a}_x + \hat{a}_z)e^{-j\frac{\pi \times 10^4(x-z)}{3\sqrt{2}}}$  V/m      (B)  $-\frac{E_0}{\sqrt{2}}(\hat{a}_x + \hat{a}_z)e^{j\frac{\pi \times 10^4 z}{3}}$  V/m
- (C)  $0.44\frac{E_0}{\sqrt{2}}(\hat{a}_x + \hat{a}_z)e^{-j\frac{\pi \times 10^4(x-z)}{3\sqrt{2}}}$  V/m      (D)  $\frac{E_0}{\sqrt{2}}(\hat{a}_x + \hat{a}_z)e^{-j\frac{\pi \times 10^4(x+z)}{3}}$  V/m

**Answer: (A)**

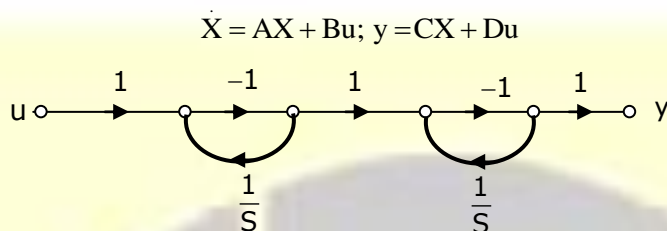**Statement for Linked Answer Questions: 54 & 55**

The state diagram of a system is shown below. A system is described by the state-variable equations



54. The state-variable equations of the system shown in the figure above are

(A)  $\dot{X} = \begin{bmatrix} -1 & 0 \\ 1 & -1 \end{bmatrix} X + \begin{bmatrix} -1 \\ 1 \end{bmatrix} u$   
 $y = [1 \ -1]X + u$

(B)  $\dot{X} = \begin{bmatrix} -1 & 0 \\ -1 & -1 \end{bmatrix} X + \begin{bmatrix} -1 \\ 1 \end{bmatrix} u$   
 $y = [-1 \ -1]X + u$

(C)  $\dot{X} = \begin{bmatrix} -1 & 0 \\ -1 & -1 \end{bmatrix} X + \begin{bmatrix} -1 \\ 1 \end{bmatrix} u$   
 $y = [1 \ -1]X - u$

(D)  $\dot{X} = \begin{bmatrix} -1 & -1 \\ 0 & -1 \end{bmatrix} X + \begin{bmatrix} -1 \\ 1 \end{bmatrix} u$   
 $y = [-1 \ -1]X - u$

**Answer: (A)**

55. The state transition matrix  $e^{At}$  of the system shown in the figure above is

(A)  $\begin{bmatrix} e^{-t} & 0 \\ te^{-t} & e^{-t} \end{bmatrix}$

(B)  $\begin{bmatrix} e^{-t} & 0 \\ -te^{-t} & e^{-t} \end{bmatrix}$

(C)  $\begin{bmatrix} e^{-t} & 0 \\ e^{-t} & e^{-t} \end{bmatrix}$

(D)  $\begin{bmatrix} e^{-t} & -te^{-t} \\ 0 & e^{-t} \end{bmatrix}$

**Answer: (A)**



Follow us @



For more details visit [gateforumonline.com](http://gateforumonline.com)