

www.gateforumonline.com



GATE PREVIOUS YEAR SOLVED PAPERS

Electronics & Telecommunications Previous Year Solved Papers

GATEFORUM Pioneers in Digital courses for GATE since 2008 has long history of training students through innovative courses. Currently GATEFORUM offers a wide range of courses from eGATE, GATE Online, Gdrive to Online TarGATE. Since inception, we have trained more 3,00,000 students since inception.

For more details visit gateforumonline.com

GATEFORUM Engineering Success

EC-GATE-2016, SET-2|

www.gateforumonline.com

GENERAL APTITUDE <u>**Q. No. 1 – 5 Carry One Mark Each**</u>

1. Based on the given statements, select the appropriate option with respect to grammar and usage.

Statements: (i) The height of Mr. X is 6 feet.

(ii) The height of Mr. Y is 5 feet.

(A) Mr. X is longer than Mr. Y

(B) Mr. X is more elongated than Mr. Y

(C) Mr. X is taller than Mr. Y

(D) Mr. X is lengthier than Mr. Y

Answer: (C)

2. The students ______ the teacher on teachers' day for twenty years of dedicated teaching.

A	nswer:	(B)		
	(C)	fantasized	(D)	facilitated
	(A)	facilitated	(B)	felicitated

3. After India's cricket world cup victory in 1985, Shrotria who was playing both tennis and cricket till then,

decided to concentrate only on cricket. And the rest is history.

What does the underlined phrase mean in this context?

- (A) history will rest in peace (B) rest is recorded in history books
- (C) rest is well known (D) rest is archaic

Answer: (C)

	TEFORUM neering Success	E	C-GATE-2016,	SET-2	www.gateforumonline.com			
4. Given $(9 \text{ inches})^{\frac{1}{2}} = (0.25 \text{ yards})^{\frac{1}{2}}$, which one of the following statements is TRUE?								
(A	A) $3 \text{ inches} = 0.$	5 yards	(B) 9	θ inches = 1.5 yards				
(0	C) 9 inches = 0 .	25 yards	(D) 8	31 inches = 0.0625 yar	ds			
Answer	: (C)							
5. S, ot 12	5. S, M, E and F are working in shifts in a team to finish a project. M works with twice the efficiency of others but for half as many days as E worked. S and M have 6 hour shifts in a day, whereas E and F have 12 hours shifts. What is the ratio of contribution of M to contribution of E in the project?							
(A	A) 1:1	(B) 1:2	(C) 1	l:4 (D)	2:1			
Answer	: (B)							
6. TI	6. The Venn diagram shows the preference of the student population for leisure activities. $ \frac{\text{Read}}{13 12 19} \frac{\text{Watch TV}}{19 19} $ Play sports							
	rom the data give: (A) 44	(B) 51	s who like to re (C)	ad books or play sport	108			
Answer	·) ·· ·· ·· ·· ·· ·· ·· ·· ·· ·· ·· ·· ·			(D)	100			
	© All rights reserved by Thi	nkcell Learning Solutions Pvt. Ltd. No pa	art of this booklet may be	reproduced or utilized in any form wit	thout the written permission.			

GATEFORUM Engineering Success

Which of the following can be logically inferred from the above statements? (i) Social science disciplines have become obsolete. (ii) Social science disciplines always promote colonialism. (iv) Social science must maintain disciplinary boundaries. (A) (ii) only (C) (iii) and (iv) only (B) (i) answer: (A) 8. Two and a quarter hours back, when seen in a mirror, the reflection of a wall clock without number markings seemed to show 1:30. What is the actual current time shown by the clock? (A) (A) 8. Two and a quarter from the same location. M travels 10 km East and then 10 km North-East. N travels 5 km South and then 4 km South-East. What is the shortest distance (in km) between M and N at the end of their travel? (A) (A) 18.60 (B) 22.50 (C) 20.61 (D) 25.00 Answer: (C)	7.	•	Social science disciplines were in existence in an amorphous form until the colonial period when they were institutionalized. In varying degrees, they were intended to further the colonial interest. In the time of globalization and the economic rise of postcolonial countries like India, conventional ways of knowledge production have become obsolete.						
 (i) Social science disciplines have become obsolete. (ii) Social science disciplines had a pre-colonial origin. (iii) Social science disciplines always promote colonialism. (iv) Social science must maintain disciplinary boundaries. (A) (ii) only (B) (i) and (iii) only (C) (ii) and (iv) only (D) (iii) and (iv) only Answer: (A) 8. Two and a quarter hours back, when seen in a mirror, the reflection of a wall clock without number markings seemed to show 1:30. What is the actual current time shown by the clock? (A) 8:15 (B) 11:15 (C) 12:15 (D) 12:45 Answer: (D) 9. M and N start from the same location. M travels 10 km East and then 10 km North-East. N travels 5 km South and then 4 km South-East. What is the shortest distance (in km) between M and N at the end of their travel? (A) 18.60 (B) 22.50 (C) 20.61 (D) 25.00 Answer: (C) 10. A wire of length 340 mm is to be cut into two parts. One of the parts is to be made into a square and the other into a rectangle where sides are in the ratio of 1:2. What is the length of the side of the square (in mm) such that the combined area of the square and the rectangle is a MINIMUM? (A) 30 (B) 40 (C) 120 (D) 180 			Whic	h of the following c	an be logically infer	red from th	e above statements	?	
 (ii) Social science disciplines had a pre-colonial origin. (iii) Social science disciplines always promote colonialism. (iv) Social science must maintain disciplinary boundaries. (A) (ii) only (B) (i) and (iii) only (C) (ii) and (iv) only (D) (iii) and (iv) only Answer: (A) 8. Two and a quarter hours back, when seen in a mirror, the reflection of a wall clock without number markings seemed to show 1:30. What is the actual current time shown by the clock? (A) 8:15 (B) 11:15 (C) 12:15 (D) 12:45 Answer: (D) 9. M and N start from the same location. M travels 10 km East and then 10 km North-East. N travels 5 km South and then 4 km South-East. What is the shortest distance (in km) between M and N at the end of their travel? (A) 18.60 (B) 22.50 (C) 20.61 (D) 25.00 Answer: (C) 10. A wire of length 340 mm is to be cut into two parts. One of the parts is to be made into a square and the other into a rectangle where sides are in the ratio of 1:2. What is the length of the side of the square (in mm) such that the combined area of the square and the rectangle is a MINIMUM? (A) 30 (B) 40 (C) 120 (D) 180 		(i) Social science disciplines have become obsolete.							
 (iii) Social science disciplines always promote colonialism. (iv) Social science must maintain disciplinary boundaries. (A) (ii) only (B) (i) and (iii) only (C) (ii) and (iv) only (D) (iii) and (iv) only Answer: (A) 8. Two and a quarter hours back, when seen in a mirror, the reflection of a wall clock without number markings seemed to show 1:30. What is the actual current time shown by the clock? (A) 8:15 (B) 11:15 (C) 12:15 (D) 12:45 Answer: (D) 9. M and N start from the same location. M travels 10 km East and then 10 km North-East. N travels 5 km South and then 4 km South-East. What is the shortest distance (in km) between M and N at the end of their travel? (A) 18.60 (B) 22.50 (C) 20.61 (D) 25.00 Answer: (C) 10. A wire of length 340 mm is to be cut into two parts. One of the parts is to be made into a square and the other into a rectangle where sides are in the ratio of 1:2. What is the length of the side of the square (in mm) such that the combined area of the square and the rectangle is a MINIMUM? (A) 30 (B) 40 (C) 120 (D) 180 			(ii)	Social science disc	ciplines had a pre-col	lonial origii	1.		
 (iv) Social science must maintain disciplinary boundaries. (A) (ii) only (B) (i) and (iii) only (C) (ii) and (iv) only (D) (iii) and (iv) only (D) (I) (I) (I) (I) (I) (I) (I) (I) (I) (I			(iii)	Social science disc	ciplines always prom	ote colonia	lism.		
 (A) (ii) only (B) (i) and (iii) only (D) (iii) and (iv) only Answer: (A) 8. Two and a quarter hours back, when seen in a mirror, the reflection of a wall clock without number markings seemed to show 1:30. What is the actual current time shown by the clock? (A) 8:15 (B) 11:15 (C) 12:15 (D) 12:45 Answer: (D) 9. M and N start from the same location. M travels 10 km East and then 10 km North-East. N travels 5 km South and then 4 km South-East. What is the shortest distance (in km) between M and N at the end of their travel? (A) 18.60 (B) 22.50 (C) 20.61 (D) 25.00 Answer: (C) 10. A wire of length 340 mm is to be cut into two parts. One of the parts is to be made into a square and the other into a rectangle where sides are in the ratio of 1:2. What is the length of the side of the square (in mm) such that the combined area of the square and the rectangle is a MINIMUM? (A) 30 (B) 40 (C) 120 (D) 180 			(IV)	Social science mus	st maintain disciplina	ary boundar	ies.		
 (C) (ii) and (iv) only (D) (iii) and (iv) only Answer: (A) 8. Two and a quarter hours back, when seen in a mirror, the reflection of a wall clock without number markings seemed to show 1:30. What is the actual current time shown by the clock? (A) 8:15 (B) 11:15 (C) 12:15 (D) 12:45 Answer: (D) 9. M and N start from the same location. M travels 10 km East and then 10 km North-East. N travels 5 km South and then 4 km South-East. What is the shortest distance (in km) between M and N at the end of their travel? (A) 18.60 (B) 22.50 (C) 20.61 (D) 25.00 Answer: (C) 10. A wire of length 340 mm is to be cut into two parts. One of the parts is to be made into a square and the other into a rectangle where sides are in the ratio of 1:2. What is the length of the side of the square (in mm) such that the combined area of the square and the rectangle is a MINIMUM? (A) 30 (B) 40 (C) 120 (D) 180 Answer: (B) 			(A)	(ii) only		(B)	(i) and (iii) only		
Answer: (A) 8. Two and a quarter hours back, when seen in a mirror, the reflection of a wall clock without number markings seemed to show 1:30. What is the actual current time shown by the clock? (A) 8:15 (B) 11:15 (C) 12:15 (D) 12:45 Answer: (D)			(C)	(ii) and (iv) only		(D)	(iii) and (iv) only		
 8. Two and a quarter hours back, when seen in a mirror, the reflection of a wall clock without number markings seemed to show 1:30. What is the actual current time shown by the clock? (A) 8:15 (B) 11:15 (C) 12:15 (D) 12:45 9. M and N start from the same location. M travels 10 km East and then 10 km North-East. N travels 5 km South and then 4 km South-East. What is the shortest distance (in km) between M and N at the end of their travel? (A) 18.60 (B) 22.50 (C) 20.61 (D) 25.00 9. A wire of length 340 mm is to be cut into two parts. One of the parts is to be made into a square and the other into a rectangle where sides are in the ratio of 1:2. What is the length of the side of the square (in mm) such that the combined area of the square and the rectangle is a MINIMUM? (A) 30 (B) 40 (C) 120 (D) 180 	A	nswe	er:	(A)					
 8. Two and a quarter hours back, when seen in a mirror, the reflection of a wall clock without number markings seemed to show 1:30. What is the actual current time shown by the clock? (A) 8:15 (B) 11:15 (C) 12:15 (D) 12:45 9. M and N start from the same location. M travels 10 km East and then 10 km North-East. N travels 5 km South and then 4 km South-East. What is the shortest distance (in km) between M and N at the end of their travel? (A) 18.60 (B) 22.50 (C) 20.61 (D) 25.00 Answer: (C) 10. A wire of length 340 mm is to be cut into two parts. One of the parts is to be made into a square and the other into a rectangle where sides are in the ratio of 1:2. What is the length of the side of the square (in mm) such that the combined area of the square and the rectangle is a MINIMUM? (A) 30 (B) 40 (C) 120 (D) 180 									
 markings seemed to show 1:30. What is the actual current time shown by the clock? (A) 8:15 (B) 11:15 (C) 12:15 (D) 12:45 Answer: (D) 9. M and N start from the same location. M travels 10 km East and then 10 km North-East. N travels 5 km South and then 4 km South-East. What is the shortest distance (in km) between M and N at the end of their travel? (A) 18.60 (B) 22.50 (C) 20.61 (D) 25.00 Answer: (C) 10. A wire of length 340 mm is to be cut into two parts. One of the parts is to be made into a square and the other into a rectangle where sides are in the ratio of 1:2. What is the length of the side of the square (in mm) such that the combined area of the square and the rectangle is a MINIMUM? (A) 30 (B) 40 (C) 120 (D) 180 	8.		Two	and a quarter hour	s back, when seen	in a mirro	r, the reflection of	a wall cloc	k without number
(A) 8:15 (B) 11:15 (C) 12:15 (D) 12:45 Answer: (D) 9. M and N start from the same location. M travels 10 km East and then 10 km North-East. N travels 5 km South and then 4 km South-East. What is the shortest distance (in km) between M and N at the end of their travel? (A) 18.60 (B) 22.50 (C) 20.61 (D) 25.00 Answer: (C) (C) 20.61 (D) 25.00 Io. A wire of length 340 mm is to be cut into two parts. One of the parts is to be made into a square and the other into a rectangle where sides are in the ratio of 1:2. What is the length of the side of the square (in mm) such that the combined area of the square and the rectangle is a MINIMUM? (A) 30 (B) 40 (C) 120 (D) 180 Answer: (B) (C) 120 (D) 180 (D) 180			mark	ings seemed to shov	v 1:30. What is the a	ctual currer	nt time shown by th	ne clock?	
 Answer: (D) 9. M and N start from the same location. M travels 10 km East and then 10 km North-East. N travels 5 km South and then 4 km South-East. What is the shortest distance (in km) between M and N at the end of their travel? (A) 18.60 (B) 22.50 (C) 20.61 (D) 25.00 Answer: (C) 10. A wire of length 340 mm is to be cut into two parts. One of the parts is to be made into a square and the other into a rectangle where sides are in the ratio of 1:2. What is the length of the side of the square (in mm) such that the combined area of the square and the rectangle is a MINIMUM? (A) 30 (B) 40 (C) 120 (D) 180 			(A)	8:15	(B) 11:15	(C)	12:15	(D) 12:4	5
 9. M and N start from the same location. M travels 10 km East and then 10 km North-East. N travels 5 km South and then 4 km South-East. What is the shortest distance (in km) between M and N at the end of their travel? (A) 18.60 (B) 22.50 (C) 20.61 (D) 25.00 Answer: (C) 10. A wire of length 340 mm is to be cut into two parts. One of the parts is to be made into a square and the other into a rectangle where sides are in the ratio of 1:2. What is the length of the side of the square (in mm) such that the combined area of the square and the rectangle is a MINIMUM? (A) 30 (B) 40 (C) 120 (D) 180 Answer: (B) 	A	nswe	er:	(D)					
 9. M and N start from the same location. M travers to kin East and then to kin North-East. N travers 3 kin South and then 4 km South-East. What is the shortest distance (in km) between M and N at the end of their travel? (A) 18.60 (B) 22.50 (C) 20.61 (D) 25.00 Answer: (C) 10. A wire of length 340 mm is to be cut into two parts. One of the parts is to be made into a square and the other into a rectangle where sides are in the ratio of 1:2. What is the length of the side of the square (in mm) such that the combined area of the square and the rectangle is a MINIMUM? (A) 30 (B) 40 (C) 120 (D) 180 Answer: (B) 	0		Mon	d N start from the	one location M too	vala 10 km	East and than 10	Im Nouth E	at N travels 5 km
 in and their 4 km South-Last. What is the shortest distance (in km) between M and A at the end of their travel? (A) 18.60 (B) 22.50 (C) 20.61 (D) 25.00 Answer: (C) 10. A wire of length 340 mm is to be cut into two parts. One of the parts is to be made into a square and the other into a rectangle where sides are in the ratio of 1:2. What is the length of the side of the square (in mm) such that the combined area of the square and the rectangle is a MINIMUM? (A) 30 (B) 40 (C) 120 (D) 180 Answer: (B) 	у.		Ni an	and then 4 km So	with-East What is the	ne shortest	distance (in km) b	etween M a	N at the end of
 (A) 18.60 (B) 22.50 (C) 20.61 (D) 25.00 Answer: (C) 10. A wire of length 340 mm is to be cut into two parts. One of the parts is to be made into a square and the other into a rectangle where sides are in the ratio of 1:2. What is the length of the side of the square (in mm) such that the combined area of the square and the rectangle is a MINIMUM? (A) 30 (B) 40 (C) 120 (D) 180 Answer: (B) 			their	travel?	uui-Last. What is u	ie shortest	distance (in kin) b		id iv at the chd of
 (A) 18.00 (B) 22.50 (C) 20.01 (D) 25.00 Answer: (C) 10. A wire of length 340 mm is to be cut into two parts. One of the parts is to be made into a square and the other into a rectangle where sides are in the ratio of 1:2. What is the length of the side of the square (in mm) such that the combined area of the square and the rectangle is a MINIMUM? (A) 30 (B) 40 (C) 120 (D) 180 Answer: (B) 			(A)	18.60	(B) 22.50	(\mathbf{C})	20.61	(D) 25 (0
 Answer: (C) 10. A wire of length 340 mm is to be cut into two parts. One of the parts is to be made into a square and the other into a rectangle where sides are in the ratio of 1:2. What is the length of the side of the square (in mm) such that the combined area of the square and the rectangle is a MINIMUM? (A) 30 (B) 40 (C) 120 (D) 180 Answer: (B) 			(Л)	10.00	(D) 22.50	(C)	20.01	(D) 25.0	0
 10. A wire of length 340 mm is to be cut into two parts. One of the parts is to be made into a square and the other into a rectangle where sides are in the ratio of 1:2. What is the length of the side of the square (in mm) such that the combined area of the square and the rectangle is a MINIMUM? (A) 30 (B) 40 (C) 120 (D) 180 Answer: (B)	A 	nswe	er:	(C)					
other into a rectangle where sides are in the ratio of 1:2. What is the length of the side of the square (in mm) such that the combined area of the square and the rectangle is a MINIMUM? (A) 30 (B) 40 (C) 120 (D) 180 Answer: (B)	1	10. A wire of length 340 mm is to be cut into two parts. One of the parts is to be made into a square and the							
(A) 30 (B) 40 (C) 120 (D) 180 Answer: (B)		other into a rectangle where sides are in the ratio of 1:2. What is the length of the side of the square (in mm) such that the combined area of the square and the rectangle is a MINIMUM?					e of the square (in		
Answer: (B)			(A)	30	(B) 40	(C)	120	(D) 180	
	A	nswe	er:	(B)					
© All rights reserved by Thinkcell Learning Solutions Pvt. Ltd. No part of this booklet may be reproduced or utilized in any form without the written permission.			© Al	I rights reserved by Thinkcell Lea	arning Solutions Pvt. Ltd. No part	of this booklet may	be reproduced or utilized in an	y form without the wr	tten permission.



www.gateforumonline.com

ELECTRONICS AND COMMUNICATION ENGINEERING

Q. No. 1 – 25 Carry One Mark Each

1. The value of x for which the matrix $A = \begin{bmatrix} 3 & 2 & 4 \\ 9 & 7 & 13 \end{bmatrix}$ has zero a	s an eigenvalue is					
$\begin{bmatrix} -6 & -4 & -9 + x \end{bmatrix}$ Answer: (1)						
2. Consider the complex valued function $f(z) = 2z^3 + b z ^2$ where z is a consider the complex valued function $f(z) = 2z^3 + b z ^2$ where z is a constant of the second seco	complex variable.					
The value of b for which the function $f(z)$ is analytic is						
Answer: (0)						
3. As x varies from -1 to $+3$, which one of the following descr	ibes the behaviour of the function					
$f(x) = x^3 - 3x^2 + 1?$						
(A) f(x) increase monotonically						
(B) $f(x)$ increases, then decreases and increases again						
(C) $f(x)$ decreases, then increases and decreases again	C) $f(x)$ decreases, then increases and decreases again					
(D) f(x) increases and then decreases						
Answer: (B)						
$1 \qquad \qquad$	n is in rediance?					
4. How many distinct values of x satisfy the equation $\sin(x) = x/2$, where (A) 1 (B) 2	e x is in radians?					
$(A) I \qquad (B) 2$						
Answer: (C)	Answer: (C)					
© All rights reserved by Thinkcell Learning Solutions Pvt. Ltd. No part of this booklet may be reproduced or util	zed in any form without the written permission.					







www.gateforumonline.com

Answer: (D)

9.

EC-GATE-2016, SET-2 www.gateforumonline.com A long-channel NMOS transistor is biased in the linear region with $V_{DS} = 50 \text{mV}$ and is used as a 12. resistance. Which one of the following statements is NOT correct? If the device width W is increased, the resistance decreases. (A) (B) If the threshold voltage is reduced, the resistance decreases. If the device length L is increased, the resistance increases. (C) (D) If V_{GS} is increased, the resistance increases. **Answer: (D)**

13. Assume that the diode in the figure has $V_{on} = 0.7V$, but is otherwise ideal.



The magnitude of the current i_2 (in mA) is equal to _____

Answer: (0.25)

14. Resistor R_1 in the circuit below figure has been adjusted so that $I_1 = 1$ mA.



The bipolar transistors Q_1 and Q_2 are perfectly matched and have very high current gain, so their base currents are negligible. The supply voltage V_{cc} is 6 V. The thermal voltage kT/q is 26 mV.

The value of $R_2(in \Omega)$ for which $I_2 = 100 \ \mu A$ is _____.

Answer: (598.65)

GATEFORUN

- **15.** Which one of the following statements is correct about an ac-coupled common-emitter amplifier operating in the mid-band region?
 - (A) The device parasitic capacitances behave like open circuits, whereas coupling and by pass capacitances behave like short circuits.
 - (B) The device parasitic capacitances, coupling capacitances and bypass capacitances behave like open circuits.
 - (C) The device parasitic capacitances, coupling capacitances and bypass capacitances behave like short circuits.
 - (D) The device parasitic capacitances behave like short circuits, whereas coupling and bypass capacitances behave like open circuits.

Answer: (A)

16. Transistor geometries in a CMOS inverter have been adjusted to meet the requirement for worst case charge and discharge times for driving a load capacitor C. This design is to be converted to that of a NOR circuit in the same technology, so that its worst case charge and discharge times while driving the same capacitor are similar. The channel lengths of all transistors are to be kept unchanged. Which one of the following statements is correct?





- (A) Widths of PMOS transistors should be doubled, while widths of NMOS transistors should be halved.
- (B) Widths of PMOS transistors should be doubled, while widths of NMOS transistors should not be changed.
- (C) Widths of PMOS transistors should be halved, while widths of NMOS transistors should not be changed.
- (D) Widths of PMOS transistors should be unchanged, while widths of NMOS transistors should be halved.

Answer: (B)

17. Assume that all the digital gates in the circuit shown in the figure are ideal, the resistor $R = 10k\Omega$ and the supply voltage is 5V. The D flip-flops D_1 , D_2 , D_3 , D_4 and D_5 are initialized with logicvalues 0,1,0,1 and 0, respectively. The clock has a 30% duty cycle.



The average power dissipated (in mW) in the resistor R is _____.

Answer: (1.5)

18. A 4:1 multiplexer is to be used for generating the output carry of a full adder. A and B are the bits to be added while C_{in} is the input carry and C_{out} is the output carry. A and B are to be used as the select bits with A being the more significant select bit. Which one of the following statements correctly describes the choice of signals to be connected to the inputs I_0 , I_1 , I_2 and I_3 so that the output is C_{out} ?





22. A speech signal is sampled at 8 kHz and encoded into PCM format using 8 bits/sample. The PCM data is transmitted through a baseband channel via 4-level PAM. The minimum bandwidth (in Hz) required for transmission is _____.

Answer: (16000)



www.gateforumonline.com



GATE REFRESHER COURSE

Electronics & Telecommunications Engineering

GATEFORUM Pioneers in Digital courses for GATE since 2008 offers **GATE refresher course** giving you access to video solutions for previous 11 years GATE questions and Topic-wise formula Compendium (Handbook).

Enroll now and get 20% discount use Promo Code GATEPAPERS

For more details visit gateforumonline.com

	Engineering Success	GATE-2016, SET-2	www.gateforumonline.com				
23.	A uniform and constant magnetic field $B = \hat{z}B$ exists in the \hat{z} direction in vacuum. A particle of mass with a small charge q is introduced into this region with an initial velocity $v = \hat{x}v_x + \hat{z}v_z$. Given that B, 1 q, v_x and v_z are all non-zero, which one of the following describes the eventual trajectory of the particle?						
	(A) Helical motion in the \hat{z} direction	(B) Circular motion in th	ne xy plane				
	(C) Linear motion in the \hat{z} direction	(D) Linear motion in the	$\hat{\mathbf{x}}$ direction				
An	nswer: (A)						
24	. Let the electric field vector of a plane electr	omagnetic wave propagating in	a homogenous medium be				
	expressed as $E = \hat{x}E_x e^{-j(\omega t - \beta z)}$, where the j	propagation constant β is a	function of the angular				
	frequency ω . Assume that $\beta(\omega)$ and E_x are known	own and are real. From the info	rmation available, which one				
	of the following CANNOT be determined?						
	(A) The type of polarization of the wave	(B) The group velocity of t	the wave				
	(C) The phase velocity of the wave	(D) The power flux through	h the $z = 0$ plane				
An	nswer: (D)						

25. Light from free space is incident at an angle θ_i to the normal of the facet of a step-index large core optical fibre. The core and cladding refractive indices are $n_1 = 1.5$ and $n_2 = 1.4$, respectively.

•

Free space	n ₂ (cladding)	
θ	n ₁ (core)	\Box
Light		\neg

The maximum value of θ_i (in degrees) for which the incident light will be guided in the core of the fibre is

Answer: (32.58)

GATEFORUM

EC-GATE-2016, SET-2 www.gateforumonline.com

Q. No. 26 - 55 Carry Two Marks Each

26. The ordinary differential equation

 $\frac{dx}{dt} = -3x + 2$, with x(0) = 1

is to be solved using the forward Euler method. The largest time step that can be used to solve the equation without making the numerical solution unstable is _____.

Answer: (0.66)

Suppose C is the closed curve defined as the circle $x^2 + y^2 = 1$ with C oriented anti-clockwise. 27.

The value of $\oint (xy^2 dx + x^2 y dy)$ over the curve C equals _____.

Answer: (0)

28. Two random variables X and Y are distributed according to

$$f_{X,Y}(x,y) = \begin{cases} (x+y), & 0 \le x \le 1, 0 \le y \le 1\\ 0, & \text{otherwise} \end{cases}$$

The probability $P(X+Y \le 1)$ is _

Answer: (0.333)

29. The matrix
$$A = \begin{bmatrix} a & 0 & 3 & 7 \\ 2 & 5 & 1 & 3 \\ 0 & 0 & 2 & 4 \\ 0 & 0 & 0 & b \end{bmatrix}$$
 has det(A) = 100 and trace(A) = 14.

The value of |a - b| is _____.

Answer: (3)



31. In the circuit shown in the figure, the magnitude of the current (in amperes) through R_2 is______.



Answer: (5)

32. A continuous-time filter with transfer function $H(s) = \frac{2s+6}{s^2+6s+8}$ is converted to a discrete time filter with

transfer function $G(z) = \frac{2z^2 - 0.5032z}{z^2 - 0.5032z + k}$ so that the impulse response of the continuous-time filter, sampled at 2 Hz, is identical at the sampling instants to the impulse response of the discrete time filter. The value of k is ______.

Answer: (0.049)

GATEFORUM EC-GATE-2016, SET-2 www.gateforumonline.com 33. The Discrete Fourier Transform (DFT) of the 4-point sequence $x[n] = {x[0], x[1], x[2], x[3]} = {3, 2, 3, 4}$ is $X[k] = \{X[0], X[1], X[2], X[3]\} = \{12, 2j, 0, -2j\}.$ If $X_1[k]$ is the DFT of the 12-point sequence $x_1[n] = \{3,0,0,2,0,0,3,0,0,4,0,0\}$, the value of Answer: (6) The switch S in the circuit shown has been closed for a long time. It is opened at time t = 0 and remains 34. open after that. Assume that the diode has zero reverse current and zero forward voltage drop. t=0 1Ω MM 10 μ F**=** 1 mH 🔶 10 V The steady state magnitude of the capacitor voltage V_c (in volts) is _____ (100)**Answer:** A voltage V_G is applied across a MOS capacitor with metal gate and p-type silicon substrate 35. at T = 300K. The inversion carrier density (in number of carriers per unit area) for $V_G = 0.8$ V

is 2×10^{11} cm⁻². For V_G = 1.3V, the inversion carrier density is 4×10^{11} cm⁻². What is the value of the inversion carrier density for V = 1.8 V?

(A)
$$4.5 \times 10^{11} \text{ cm}^{-2}$$
 (B) $6.0 \times 10^{11} \text{ cm}^{-2}$ (C) $7.2 \times 10^{11} \text{ cm}^{-2}$ (D) $8.4 \times 10^{11} \text{ cm}^{-2}$
Answer: (B)

36. Consider avalanche breakdown in a silicon p^+n junction. The n-region is uniformly doped with a donor density N_D. Assume that breakdown occurs when the magnitude of the electric field at any point in the device becomes equal to the critical field E_{crit} . Assume E_{crit} to be independent of N_D. If the built-in voltage of the p^+n junction is much smaller than the breakdown voltage, V_{BR}, the relationship between V_{BR} and N_D is given by

(A)
$$V_{BR} \times \sqrt{N_D} = \text{constant}$$
 (B) $N_D \times \sqrt{V_{BR}} = \text{constant}$
(C) $N_D \times V_{BR} = \text{constant}$ (D) $N_D / V_{BR} = \text{constant}$

Answer: (C)

GATEFORUM

37. Consider a region of silicon devoid of electrons and holes, with an ionized donor density of $N_d^+ = 10^{17} \text{ cm}^{-3}$. The electric field at x = 0 is 0 V/cm and the electric field at x = L is 50 kV/cm in the positive x direction. Assume that the electric field is zero in the y and z directions at all points.



Given $q = 1.6 \times 10^{-19}$ coulomb, $\epsilon_0 = 8.85 \times 10^{-14}$ F/cm, $\epsilon_r = 11.7$ for silicon, the value of *L* is _____ nm.

Answer: (32.37)

38. Consider a long-channel NMOS transistor with source and body connected together. Assume that the electron mobility is independent of V_{GS} and V_{DS} . Given,

 $g_{\rm m} = 0.5 \,\mu A/V \text{ for } V_{\rm DS} = 50 \text{ mV and } V_{\rm GS} = 2 \text{ V},$ $g_{\rm d} = 8 \,\mu A/V \text{ for } V_{\rm GS} = 2 \text{ V and } V_{\rm DS} = 0 \text{ V},$

where
$$g_m = \frac{\partial I_D}{\partial V_{GS}}$$
 and $g_d = \frac{\partial I_D}{\partial V_{DS}}$

The threshold voltage (in volts) of the transistor is ______.

Answer: (1.2)

[©] All rights reserved by Thinkcell Learning Solutions Pvt. Ltd. No part of this booklet may be reproduced or utilized in any form without the written permission.

39. The figure shows a half-wave rectifier with a 475μ F filter capacitor. The load draws a constant current $I_0=1$ A from the rectifier. The figure also shows the input voltage V_i , the output voltage V_C and the peak-to-peak voltage ripple V on V_C . the input voltage V_i is a triangle-wave with an amplitude of 10 V and a period of 1ms.



40. In the op-amp circuit shown, the Zener diodes Z_1 and Z_2 clamp the output voltage V_0 to +5V or -5V. The switch S is initially closed and is opened at time t = 0.



The time $t = t_1$ (in seconds) at which V_0 changes state is_____

Answer: (0.798)

GATEFORUM

41. An op-amp has a finite open loop voltage gain of 100. Its input offset voltage $V_{ios} = (+5mV)$ is modeled as shown in the circuit below. The amplifier is ideal in all other respects. V_{input} is 25 mV.



- 42. An 8 Kbyte ROM with an active low Chip Select input (\overline{CS}) is to be used in an 8085 microprocessor based system. The ROM should occupy the address range 1000H to 2FFFH. The address lines are designated as A₁₅ to A₀, where A₁₅ is the most significant address bit. Which one of the following logic expressions will generate the correct (\overline{CS}) signal for this ROM?
 - (A) $A_{15} + A_{14} + (A_{13} \cdot A_{12} + \overline{A_{13}} \cdot \overline{A_{12}})$ (B) $A_{15} \cdot A_{14} \cdot (A_{13} + A_{12})$

(C)
$$\overline{A_{15}} + \overline{A_{14}} + (A_{13}.A_{12} + \overline{A_{13}}.A_{12})$$
 (D) $\overline{A_{15}} + \overline{A_{14}} + A_{13}.A_{12}$

Answer: (A)

GATEFORUM

43. In an N bit flash ADC, the analog voltage is fed simultaneously to 2^{N} – 1 comparators. The output of the comparators is then encoded to a binary format using digital circuits. Assume that the analog voltage source V_{in} (whose output is being converted to digital format) has a source resistance of 75 Ω as shown in the circuit diagram below and the input capacitance of each comparator is 8 pF.



sampling rate?

- (A) 1 megasamples per second
- (B) 6 megasamples per second
- (C) 64 megasamples per second
- (D) 256 megasamples per second

Answer: (A)

44. The state transition diagram for a finite state machine with states A, B and C, and binary inputs X,Y and Z, is shown in the figure.







48. An information source generates a binary sequence $\{\alpha_n\}$. α_n can take one of the two possible values -1 and +1 with equal probability and are statistically independent and identically distributed. This sequence is precoded to obtain another sequence $\{\beta_n\}$, as $\beta_n = \alpha_n + k \alpha_{n-3}$. The sequence $\{\beta_n\}$ is used to modulate a pulse g(t) to generate the baseband signal

$$X(t) = \sum_{n=-\infty}^{\infty} \beta_n g(t - nT), \text{ where } g(t) = \begin{cases} 1, & 0 \le t \le T \\ 0, & \text{otherwise} \end{cases}$$

If there is a null at $f = \frac{1}{3T}$ in the power spectral density of X(t), then k is _____.

Answer: (-1)

49. An ideal band-pass channel 500 Hz - 2000 Hz is deployed for communication. A modem is designed to transmit bits at the rate of 4800 bits/s using 16-QAM. The roll-off factor of a pulse with a raised cosine spectrum that utilizes the entire frequency band is ______.

Answer: (0.25)

EC-GATE-2016, SET-2] www.gateforumonline.com 50. Consider a random process X(t)=3V(t)-8, where V(t) is a zero mean stationary random process with autocorrelation R_v(τ)=4.e^{-5|τ|}. The power in X(t) is _____. Answer: (100) 51. A binary communication system makes use of the symbols "zero" and "one". There are channel errors. Consider the following events: x₀: a "zero" is transmitted x₁: a "one" is transmitted

- y₀: a "zero" is received
- y₁: a "one" is received

The following probabilities are given: $P(x_0) = \frac{1}{2}$, $P(y_0 | x_0) = \frac{3}{4}$, and $P(y_0 | x_1) = \frac{1}{2}$. The information in bits that you obtain when you learn which symbol has been received (while you know that a "zero" has been transmitted) is_____.

Answer: (0.811)

52. The parallel-plate capacitor shown in the figure has movable plates. The capacitor is charged so that the energy stored in it is E when the plate separation is d. The capacitor is then isolated electrically and the plates are moved such that the plate separation becomes 2d.



53. A lossless micro strip transmission line consists of a trace of width w. It is drawn over a practically infinite ground plane and is separated by a dielectric slab of thickness t and relative permittivity $\varepsilon_r > 1$. The inductance per unit length and the characteristic impedance of this line are L and Z₀, respectively.

EGATEFORUM



54. A microwave circuit consisting of lossless transmission lines T_1 and T_2 is shown in the figure. The plot shows the magnitude of the input reflection coefficient Γ as a function of frequency f. The phase velocity of the signal in the transmission lines is 2×10^8 m/s..



GATEFORUM Engineering Success

EC-GATE-2016, SET-2

55. A positive charge q is placed at x=0 between two infinite metal plates placed at x=-d and at x=+d respectively.

The metal plates lie in the yz plane. The charge is at rest at t=0, when a voltage +V is applied to the plate at -d and voltage -V is applied to the plate at x= +d. Assume that the quantity of the charge q is small enough that it does not disturb the field set up by the metal plates. The time that the charge q takes to reach the right plate is proportional to



