



*GATE PREVIOUS YEAR SOLVED PAPERS*  
**Electrical Engineering  
Previous Year Solved Papers**

**GATEFORUM** Pioneers in Digital courses for GATE since 2008 has long history of training students through innovative courses. Currently GATEFORUM offers a wide range of courses from eGATE, GATE Online, Gdrive to Online TarGATE. Since inception, we have trained more 3,00,000 students since inception.

**For more details visit [gateforumonline.com](http://gateforumonline.com)**

**GENERAL APTITUDE****Q. No. 1 – 5 Carry One Mark Each**

1. The passengers were angry \_\_\_\_\_ the airline staff about the delay.

(A) towards (B) on (C) with (D) about

**Answer: (C)**

2. The missing number in the given sequence 343, 1331, \_\_\_\_\_, 4913 is

(A) 4096 (B) 3375 (C) 2744 (D) 2197

**Answer: (D)**

[Click here to watch video explanation](#)

3. Newspapers are a constant source of delight and recreation for me. The \_\_\_\_\_ trouble is that I read \_\_\_\_\_ many of them.

(A) only, too (B) only, quite (C) even, too (D) even, quite

**Answer: (A)**

4. It takes two hours for a person X to mow the lawn. Y can mow the same lawn in four hours. How long (in minutes) will it take X and Y, if they work together to mow the lawn?

(A) 60 (B) 80 (C) 120 (D) 90

**Answer: (B)**

[Click here to watch video explanation](#)

5. I am not sure if the bus that has been booked will be able to \_\_\_\_\_ all the students.

(A) deteriorate (B) sit (C) accommodate (D) fill

**Answer: (C)**

**Q. No. 6 - 10 Carry Two Marks Each**

6. Given two sets  $X = \{1, 2, 3\}$  and  $Y = \{2, 3, 4\}$ , we construct a set  $Z$  of all possible fractions where the numerators belong to set  $X$  and the denominators belong to set  $Y$ . The product of elements having minimum and maximum values in the set  $Z$  is \_\_\_\_\_.

(A)  $1/12$                       (B)  $3/8$                       (C)  $1/8$                       (D)  $1/6$

**Answer: (B)**

[Click here to watch video explanation](#)

7. Consider five people-Mita, Ganga, Rekha, Lakshmi and Sana. Ganga is taller than both Rekha and Lakshmi. Lakshmi is taller than Sana. Mita is taller than Ganga.

Which of the following conclusions are TRUE?

- |                                 |                               |             |             |
|---------------------------------|-------------------------------|-------------|-------------|
| 1. Lakshmi is taller than Rekha | 2. Rekha is shorter than Mita |             |             |
| 3. Rekha is taller than Sana    | 4. Sana is shorter than Ganga |             |             |
| (A) 3 only                      | (B) 1 only                    | (C) 2 and 4 | (D) 1 and 3 |

**Answer: (C)**

[Click here to watch video explanation](#)

8. How many integers are there between 100 and 1000 all of whose digits are even?

(A) 60                      (B) 100                      (C) 90                      (D) 80

**Answer: (B)**

[Click here to watch video explanation](#)

9. An award-winning study by a group researchers suggests that men are as prone to buying on impulse as women but women feel more guilty about shopping.

Which one of the following statements can be inferred from the given text?

- (A) Many men and women indulge in buying on impulse  
(B) All men and women indulge in buying on impulse  
(C) Few men and women indulge in buying on impulse  
(D) Some men and women indulge in buying on impulse

**Answer: (D)**

[Click here to watch video explanation](#)

10. The ratio of the number of boys and girls who participated in an examination is 4:3. The total percentage of candidates who passed the examination is 80 and the percentage of girls who passed is 90. The percentage of boys who passed is \_\_\_\_\_.
- (A) 90.00                      (B) 80.50                      (C) 55.50                      (D) 72.50

**Answer: (D)**

[Click here to watch video explanation](#)

### ELECTRICAL ENGINEERING

#### Q. No. 1 –25 Carry One Mark Each

1. Given,  $V_{gs}$  is the gate-source voltage,  $V_{ds}$  is the drain source voltage, and  $V_{th}$  is the threshold voltage of an enhancement type NMOS transistor, the conditions for transistor to be biased in saturation are
- (A)  $V_{gs} < V_{th}; V_{ds} \leq V_{gs} - V_{th}$                       (B)  $V_{gs} < V_{th}; V_{ds} \geq V_{gs} - V_{th}$
- (C)  $V_{gs} > V_{th}; V_{ds} \leq V_{gs} - V_{th}$                       (D)  $V_{gs} > V_{th}; V_{ds} \geq V_{gs} - V_{th}$

**Answer: (D)**

[Click here to watch video explanation](#)

2. The mean-square of a zero-mean random process is  $\frac{kT}{C}$ , where  $k$  is Boltzmann's constant,  $T$  is the absolute temperature, and  $C$  is a capacitance. The standard deviation of the random process is
- (A)  $\frac{\sqrt{kT}}{C}$                       (B)  $\frac{kT}{C}$                       (C)  $\frac{C}{kT}$                       (D)  $\sqrt{\frac{kT}{C}}$


**Answer: (D)**

3. The parameter of an equivalent circuit of a three-phase induction motor affected by reducing the rms value of the supply voltage at the rate frequency is
- (A) magnetizing reactance                      (B) rotor leakage reactance
- (C) rotor resistance                      (D) stator resistance

**Answer: (A)**

[Click here to watch video explanation](#)

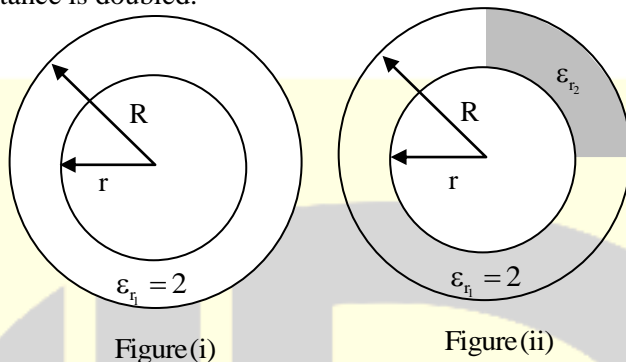4. A co-axial cylindrical capacitor shown in figure (i) has dielectric with relative permittivity  $\epsilon_{r1} = 2$ . When one-fourth portion of the dielectric is replaced with another dielectric of relative permittivity  $\epsilon_{r2}$ , as shown in figure (ii), the capacitance is doubled.



The value of  $\epsilon_{r2}$  is \_\_\_\_\_.

**Answer: (10)**


[Click here to watch video explanation](#)

5. The output voltage of a single-phase full bridge voltage source inverter is controlled by unipolar PWM with one pulse per half cycle. For the fundamental rms component of output voltage to be 75% of DC voltage, the required pulse width in degree (round off up to one decimal place) is \_\_\_\_\_.

**Answer: (112.8)**


[Click here to watch video explanation](#)

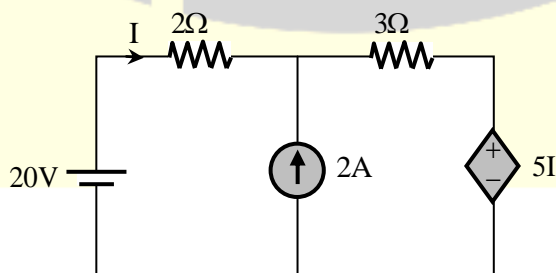6. The current  $I$  flowing in the circuit shown below in amperes (round off to one decimal place) is \_\_\_\_\_.



**Answer: (1.4)**

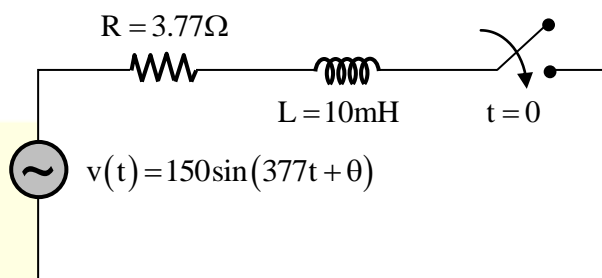7. In this circuit show below, the switch closed at  $t = 0$ . The value of  $\theta$  in degrees which will give the maximum value of DC offset of the current at the time of switching is



- (A) 60                      (B) -45                      (C) 90                      (D) -30

**Answer: (A)**

8. The total impedance of the secondary winding, leads, and burden of a 5ACT is  $0.01 \Omega$ . If the fault current is 20 times the rated primary current of the CT, the VA output of the CT is \_\_\_\_\_.

**Answer: (100)**

[Click here to watch video explanation](#)

9. A 5kVA, 50 V/100V, single-phase transformer has a secondary terminal voltage of 95V when loaded. The regulation of the transformer is

- (A) 5%                      (B) 9%                      (C) 4.5%                      (D) 1%

**Answer: (A)**

[Click here to watch video explanation](#)

10. Five alternators each rated 5MVA, 13.2 kV with 25% of reactance on its own base are connected in parallel to a busbar. The short-circuit level in MVA at the busbar is \_\_\_\_\_.

**Answer: (100)**

[Click here to watch video explanation](#)

11. A sixpulse thyristor bridge rectifier is connected to a balanced three-phase, 50 Hz AC source. Assuming that the DC output current of the rectifier is constant, the lowest harmonic component in the AC input current is

- (A) 100 Hz                      (B) 150 Hz                      (C) 250 Hz                      (D) 300 Hz

**Answer: (C)**

[Click here to watch video explanation](#)

12. The characteristic equation of a linear time-invariant (LTI) system is given by

$$\Delta(s) = s^4 + 3s^3 + 3s^2 + s + k = 0$$

The system BIBO stable if

- (A)  $k > 3$                       (B)  $0 < k < \frac{8}{9}$                       (C)  $0 < k < \frac{12}{9}$                       (D)  $k > 6$

**Answer: (B)**

13. A system transfer function is  $H(s) = \frac{a_1 s^2 + b_1 s + c_1}{a_2 s^2 + b_2 s + c_2}$ . If  $a_1 = b_1 = 0$ , and all other coefficients are positive,

the transfer function represents a

- (A) low pass filter                      (B) high pass filter  
(C) band pass filter                      (D) notch filter

**Answer: (A)**

14. The symbols,  $a$  and  $T$ , represent quantities, and  $u(t)$  is the unit step function. Which one of the following impulse responses is NOT the output of a causal linear time-invariant system?

- (A)  $e^{+at}u(t)$                       (B)  $e^{-a(t+T)}u(t)$   
(C)  $1 + e^{-at}u(t)$                       (D)  $e^{-a(t-T)}u(t)$

**Answer: (C)**

15. If  $f = 2x^3 + 3y^2 + 4z$ , the value of line integral  $\int_C \text{grad } f \cdot d\mathbf{r}$  evaluated over contour  $C$  formed by the segments  $\rightarrow(2, 6, 2) \rightarrow (2, 6, -1) \rightarrow (-3, -3, 2) \rightarrow (2, -3, 2)$  is \_\_\_\_\_.

**Answer: (139)**

[Click here to watch video explanation](#)

16. A three-phase synchronous motor draws 200 A from the line at unity power factor at rated load. Considering the same line voltage and load, the line current at a power factor of 0.5 leading is

(A) 100A                      (B) 300A                      (C) 400A                      (D) 200A

**Answer: (C)**

[Click here to watch video explanation](#)

17. The inverse Laplace transform of

$$H(s) = \frac{s+3}{s^2+2s+1} \text{ for } t \geq 0 \text{ is}$$

(A)  $3te^{-t} + e^{-t}$                       (B)  $3e^{-t}$                       (C)  $4te^{-t} + e^{-t}$                       (D)  $2te^{-t} + e^{-t}$

**Answer: (D)**

[Click here to watch video explanation](#)

18. The open loop transfer function of a unity feedback system is given by

$$G(s) = \frac{\pi e^{-0.25s}}{s},$$

In  $G(s)$  plane, the Nyquist plot of  $G(s)$  passes through the negative real axis at the point.

(A)  $(-1.5, j0)$                       (B)  $(-0.5, j0)$                       (C)  $(-0.75, j0)$                       (D)  $(-1.25, j0)$

**Answer: (B)**

19. The partial differential equation  $\frac{\partial^2 u}{\partial t^2} - C^2 \left( \frac{\partial^2 u}{\partial x^2} + \frac{\partial^2 u}{\partial y^2} \right) = 0$ ; where  $C \neq 0$  is known as

(A) Wave equation                      (B) Poisson's equation  
(C) Laplace equation                      (D) Heat equation

**Answer: (A)**

[Click here to watch video explanation](#)



20. M is a  $2 \times 2$  matrix with eigen values 4 and 9. The eigen values of  $M^2$  are

- (A) 16 and 81      (B) 2 and 3      (C) -2 and -3      (D) 4 and 9

**Answer:** (A)

[Click here to watch video explanation](#)

21. The  $Y_{bus}$  matrix of a two-bus power system having two identical parallel lines connected between them in pu is given as

$$Y_{bus} = \begin{bmatrix} -j8 & j20 \\ j20 & -j8 \end{bmatrix}.$$

The magnitude of the series reactance of each line in pu (round off up to one decimal place) is

\_\_\_\_\_.

**Answer:** (0.1)

[Click here to watch video explanation](#)

22. The rank of the matrix,  $M = \begin{bmatrix} 0 & 1 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 0 \end{bmatrix}$ , is \_\_\_\_\_.

**Answer:** (3)

[Click here to watch video explanation](#)

23. The output response of a system is denoted as  $y(t)$ , and its Laplace transform is given by

$$Y(s) = \frac{10}{s(s^2 + s + 100\sqrt{2})}.$$

The steady state value of  $y(t)$  is

- (A)  $\frac{1}{10\sqrt{2}}$       (B)  $10\sqrt{2}$       (C)  $\frac{1}{100\sqrt{2}}$       (D)  $100\sqrt{2}$

**Answer:** (A)



## *GATE REFRESHER COURSE* Electrical Engineering

**GATEFORUM** Pioneers in Digital courses for GATE since 2008 offers **GATE refresher course** giving you access to video solutions for previous 11 years GATE questions and Topic-wise formula Compendium (Handbook).

**Enroll now and get 20% discount use  
Promo Code **GATEPAPERS****

**For more details visit [gateforumonline.com](http://gateforumonline.com)**

24. A current controlled current source (CCCS) has an input impedance of  $10\Omega$  and output impedance of  $100\text{ k}\Omega$ . When this CCCS is used in a negative feedback closed loop with a loop gain of 9, the closed loop output impedance is
- (A)  $100\text{ k}\Omega$       (B)  $100\Omega$       (C)  $10\Omega$       (D)  $1000\text{ k}\Omega$

**Answer: (D)**

[Click here to watch video explanation](#)

25. Which one of the following functions is analytic in the region  $|z| \leq 1$ ?


(A)  $\frac{z^2 - 1}{z + j0.5}$       (B)  $\frac{z^2 - 1}{z + 2}$       (C)  $\frac{z^2 - 1}{z - 0.5}$       (D)  $\frac{z^2 - 1}{z}$

**Answer: (B)**

[Click here to watch video explanation](#)

Q. No. 26 - 55 Carry Two Marks Each

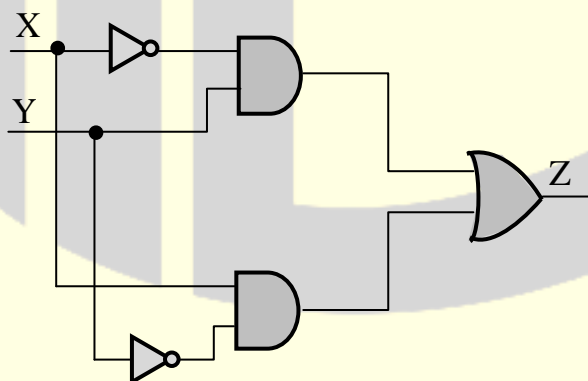
26. In the circuit shown below, X and Y are digital inputs, and Z is a digital output. The equivalent circuit is a



- (A) NAND gate      (B) NOR gate      (C) XOR gate      (D) XNOR gate

**Answer: (C)**

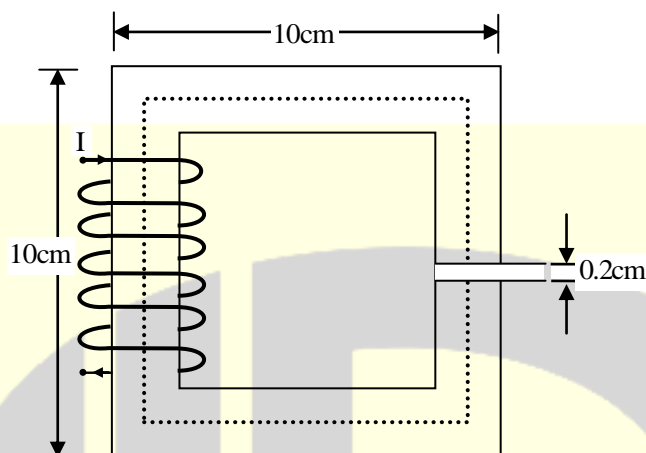27. The magnetic circuit shown below has uniform cross-sectional area and air gap of 0.2 cm. The mean path length of the core is 40 cm. Assume that leakage and fringing fluxes are negligible.



When the core relative permeability is assumed to be infinite, the magnetic flux density computed in the air gap is 1 tesla. With same Ampere-turns, if the core relative permeability is assumed to be 1000 (linear), the flux density in tesla (round off to three decimal places) calculated in the air gap is\_\_\_\_\_.

**Answer: (0.834)**

28. A delta-connected, 3.7 kW, 400 V(line), three-phase, 4-pole, 50-Hz squirrel-cage induction motor has the following equivalent circuit parameter per phase referred to the stator:  
 $R_1 = 5.39\Omega$ ,  $R_2 = 5.72\Omega$ ,  $X_1 = X_2 = 8.22\Omega$ . Neglect shunt branch in the equivalent circuit. The starting line current in amperes (round off to two decimal places) when it is connected to a 100V (line), 10 Hz, three-phase AC source is \_\_\_\_\_.

**Answer: (14.94)**


[Click here to watch video explanation](#)

29. If  $A = 2xi + 3yj + 4zk$  and  $u = x^2 + y^2 + z^2$ , then  $\text{div}(uA)$  at (1, 1, 1) is\_\_\_\_\_.

**Answer: (45)**

[Click here to watch video explanation](#)

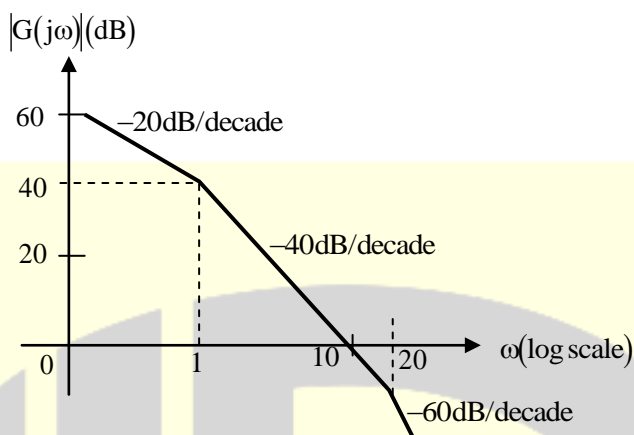30. The asymptotic Bode magnitude plot of a minimum phase transfer function  $G(s)$  is shown below.



Consider the following two statements.

**Statement I:** Transfer function  $G(s)$  has three poles and one zero.

**Statement II:** At very high frequency ( $\omega \rightarrow \infty$ ), the phase angle  $\angle G(j\omega) = -\frac{3\pi}{2}$ .

Which one of the following option is correct?

- (A) Statement I is false and statement II is true.
- (B) Both the statements are true.
- (C) Both the statements are false.
- (D) Statement I is true and statement II is false.

**Answer: (A)**

31. The transfer function of a phase lead compensator is given by  $D(s) = \frac{3\left(s + \frac{1}{aT}\right)}{\left(s + \frac{1}{T}\right)}$ . The frequency

(in rad/sec), at which  $\angle D(j\omega)$  is maximum, is

- (A)  $\sqrt{3T^2}$
- (B)  $\sqrt{\frac{3}{T^2}}$
- (C)  $\sqrt{3T}$
- (D)  $\sqrt{\frac{1}{3T^2}}$

**Answer: (D)**

32. The voltage across and the current through a load are expressed as follows

$$v(t) = -170 \sin\left(377t - \frac{\pi}{6}\right) \text{ V}$$

$$i(t) = 8 \cos\left(377t + \frac{\pi}{6}\right) \text{ A}$$

The average power in watts (round off to one decimal place) consumed by the load is \_\_\_\_\_.

**Answer: (588.89)**

33. A DC-DC buck converter operates in continuous conduction mode. It has 48 V input voltage, and it feeds a resistive load of  $24 \, \Omega$ . The switching frequency of the converter is 250 Hz. If switch-on duration is 1 ms, the load power is

(A) 12W                      (B) 6W                      (C) 48W                      (D) 24W

**Answer: (D)**

[Click here to watch video explanation](#)

34. A single-phase fully-controlled thyristor converter is used to obtain an average voltage of 180V with 10 A constant current to feed a DC load. It is fed from single-phase AC supply of 230V, 50 Hz. Neglect the source impedance. The power factor (round off to two decimal places) of AC mains is \_\_\_\_\_.

**Answer: (0.78)**

[Click here to watch video explanation](#)

35. The closed loop line integral  $\oint_{|z|=5} \frac{z^3 + z^2 + 8}{z + 2} dz$  evaluated counter-clockwise, is

(A)  $+4j\pi$                       (B)  $-4j\pi$                       (C)  $+8j\pi$                       (D)  $-8j\pi$

**Answer: (C)**

[Click here to watch video explanation](#)

36. A fully-controlled three-phase bridge converter is working from a 415V, 50 Hz, AC supply. It is supplying constant current of 100 A at 400 V to a DC load. Assume large inductive smoothing and neglect overlap.


The rms value of the AC line current in amperes (round off to two decimal places) is \_\_\_\_\_.

**Answer: (81.64)**

[Click here to watch video explanation](#)

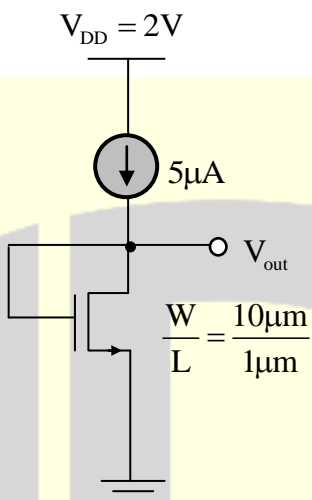37. The enhancement type MOSFET in the circuit below operates according to the square law.

$\mu_n C_{ox} = 100 \mu\text{A}/\text{V}^2$ , the threshold voltage ( $V_T$ ) is 500 mV. Ignore channel length modulation. The output voltage  $V_{out}$  is



- (A) 2V                      (B) 100 mV                      (C) 500 mV                      (D) 600 mV

**Answer: (D)**

[Click here to watch video explanation](#)

38. In a 132 kV system, the series inductance up to the point of circuit breaker location is 50 mH. The shunt capacitance at the circuit breaker terminal is  $0.05 \mu\text{F}$ . The critical value of resistance in ohms required to be connected across the circuit breaker contacts which will give no transient oscillation is\_\_\_\_\_.

**Answer: (500)**

[Click here to watch video explanation](#)

39. The probability of a resistor being defective is 0.02. There are 50 such resistors in a circuit. The probability of two or more defective resistors in the circuit (round off to two decimal places) is \_\_\_\_\_.

**Answer: (0.26)**

[Click here to watch video explanation](#)

40. The output expression for the Karnaugh map shown below is

PQ \ RS	00	01	11	10
00	0	1	1	0
01	1	1	1	1
11	1	1	1	1
10	0	0	1	1

- (A)  $Q\bar{R} + S$       (B)  $Q\bar{R} + \bar{S}$       (C)  $QR + S$       (D)  $QR + \bar{S}$

Answer: (A)

41. A periodic function  $f(t)$ , with a period of  $2\pi$ , is represented as its Fourier series,

$$f(t) = a_0 + \sum_{n=1}^{\infty} a_n \cos nt + \sum_{n=1}^{\infty} b_n \sin nt.$$

$$f(t) = \begin{cases} A \sin t, & 0 \leq t \leq \pi \\ 0, & \pi < t < 2\pi \end{cases}$$

The Fourier series coefficients  $a_1$  and  $b_1$  of  $f(t)$  are

- (A)  $a_1 = \frac{A}{\pi}; b_1 = 0$       (B)  $a_1 = \frac{A}{2}; b_1 = 0$   
(C)  $a_1 = 0; b_1 = \frac{A}{\pi}$       (D)  $a_1 = 0; b_1 = \frac{A}{2}$

Answer: (D)

42. A  $0.1\mu\text{F}$  capacitor charged to 100V is discharged through a  $1\text{ k}\Omega$  resistor. The time in ms (round off to two decimal places) required for the voltage across the capacitor to drop to 1V is \_\_\_\_\_.

Answer: (0.46)



43. A moving coil instrument having a resistance of  $10\Omega$ , gives a full-scale deflection when the current is 10 mA. What should be the value of the series resistance, so that it can be used as a voltmeter for measuring potential difference up to 100 V?

(A)  $9990\Omega$       (B)  $990\Omega$       (C)  $99\Omega$       (D)  $9\Omega$


**Answer: (A)**

44. A three-phase 50 Hz, 400 kV transmission line is 300 km long. The line inductance is 1 mH/km per phase, and the capacitance is  $0.01\mu\text{F}/\text{km}$  per phase. The line is under open circuit condition at the receiving end and energized with 400 kV at the sending end, the receiving end line voltage in kV (round off to two decimal places) will be \_\_\_\_\_.

**Answer: (418.59)**

[Click here to watch video explanation](#)

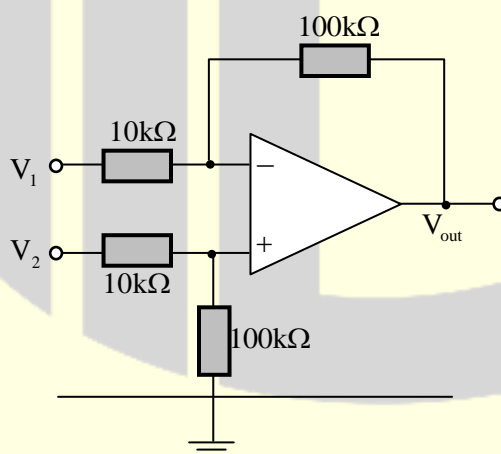45. In the circuit below, the operational amplifier is ideal. If  $V_1 = 10\text{ mV}$  and  $V_2 = 50\text{ mV}$ , the output voltage ( $V_{\text{out}}$ ) is




(A) 100 mV      (B) 600 mV      (C) 400 mV      (D) 500 mV

**Answer: (C)**

[Click here to watch video explanation](#)

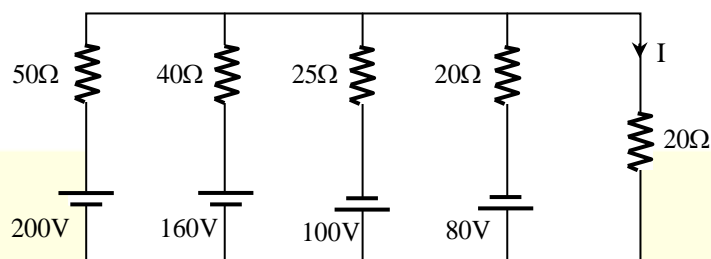46. The current  $I$  flowing in the circuit shown below in amperes is \_\_\_\_\_.



**Answer: (0)**

47. A 220V DC shunt motor takes 3A at no-load. It draws 25A when running at full-load at 1500 rpm. The armature and shunt resistances are  $0.5\Omega$  and  $220\Omega$ , respectively. The no-load speed in rpm (round off to two decimal places) is \_\_\_\_\_.

**Answer: (1579.32)**

[Click here to watch video explanation](#)

48. In a DC-DC boost converter, the duty ratio is controlled to regulate the output voltage at 48V. The input DC voltage is 24V. The output power is 120W. The switching frequency is 50kHz. Assume ideal components and a very large output filter capacitor. The converter operates at the boundary between continuous and discontinuous conduction modes. The value of the boost inductor (in  $\mu\text{H}$ ) is \_\_\_\_\_.

**Answer: (24)**

[Click here to watch video explanation](#)

49. The line currents of a three-phase four wire system are square waves with amplitude of 100A. These three currents are phase shifted by  $120^\circ$  with respect to each other. The rms value of neutral current is

(A) 100A                      (B) 0A                      (C) 300A                      (D)  $\frac{100}{\sqrt{3}}$  A

**Answer: (A)**

- 50.** A single-phase transformer of rating 25kVA, supplies a 12kW load at power factor of 0.6 lagging. The additional load at unity power factor in kW (round off to two decimal places) that may be added before this transformer exceeds its rated kVA is \_\_\_\_\_.

**Answer: (7.2)**

[Click here to watch video explanation](#)

- 51.** Consider a state-variable model of a system

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} 0 & 1 \\ -\alpha & -2\beta \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 0 \\ \alpha \end{bmatrix} r$$

$$y = \begin{bmatrix} 1 & 0 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix}$$

where  $y$  is the output, and  $r$  is the input. The damping ratio  $\xi$  and the undamped natural frequency  $\omega_n$  (rad/sec) of the system are given by

(A)  $\xi = \sqrt{\alpha}; \omega_n = \frac{\beta}{\sqrt{\alpha}}$


(B)  $\xi = \frac{\sqrt{\alpha}}{\beta}; \omega_n = \sqrt{\beta}$

(C)  $\xi = \sqrt{\beta}; \omega_n = \sqrt{\alpha}$

(D)  $\xi = \frac{\beta}{\sqrt{\alpha}}; \omega_n = \sqrt{\alpha}$

**Answer: (D)**

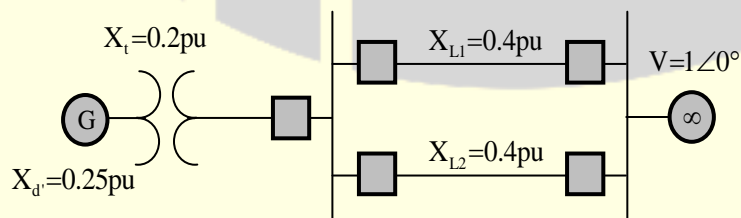- 52.** In the single machine infinite bus system shown below, the generator is delivering the real power of 0.8 pu at 0.8 power factor lagging to the infinite bus.



The power angle of the generator in degrees (round off to one decimal place) is \_\_\_\_\_.

**Answer: (20.5)**

[Click here to watch video explanation](#)

- 53.** A 30kV, 50Hz, 50MVA generator has the positive, negative, and zero sequence reactances of 0.25pu, 0.15pu, and 0.05pu, respectively. The neutral of the generator is grounded with a reactance so that the fault current for a bolted LG fault and that of a bolted three-phase fault at the generator terminal are equal. The value of grounding reactance in ohms (round off to one decimal place) is \_\_\_\_\_.

**Answer: (1.8)**

[Click here to watch video explanation](#)

- 54.** A 220V (line) three-phase, Y-connected, synchronous motor has a synchronous impedance of  $(0.25 + j2.5)\Omega$ / phase. The motor draws the rated current of 10A at 0.8 pf leading. The rms value of line-to-line internal voltage in volts (round off to two decimal places) is \_\_\_\_\_.

**Answer: (245.35)**

[Click here to watch video explanation](#)

- 55.** Consider a  $2 \times 2$  matrix  $M = \begin{bmatrix} v_1 & v_2 \end{bmatrix}$ , where  $v_1$  and  $v_2$  are the column vectors. Suppose

$M^{-1} = \begin{bmatrix} u_1^T \\ u_2^T \end{bmatrix}$  where  $u_1^T$  and  $u_2^T$  are the row vectors. Consider the following statements:

**Statement 1:**  $u_1^T v_1 = 1$  and  $u_2^T v_2 = 1$

**Statement 2:**  $u_1^T v_2 = 0$  and  $u_2^T v_1 = 0$

Which of the following options is CORRECT ?

- (A) Statement 2 is true and statement 1 is false
- (B) Statement 1 is true and statement 2 is false
- (C) Both the statements are false
- (D) Both the statements are true

**Answer: (D)**

[Click here to watch video explanation](#)



Follow us @



For more details visit [gateforumonline.com](http://gateforumonline.com)