

GATE PREVIOUS YEAR SOLVED PAPERS
**Electrical Engineering
Previous Year Solved Papers**

GATEFORUM Pioneers in Digital courses for GATE since 2008 has long history of training students through innovative courses. Currently GATEFORUM offers a wide range of courses from eGATE, GATE Online, Gdrive to Online TarGATE. Since inception, we have trained more 3,00,000 students since inception.

For more details visit gateforumonline.com

GENERAL APTITUDE**Q. No. 1 - 5 Carry One Mark Each**

1. As you grow older, an injury to your _____ may take longer to _____.
- (A) heel / heel (B) heal / heel (C) heal / heal (D) heel / heal

Answer: (D)

[Click here to watch video explanation](#)

2. In a 500 m race, P and Q have speeds in the ratio of 3 : 4. Q starts the race when P has already covered 140 m.
- What is the distance between P and Q (in m) when P wins the race?
- (A) 20 (B) 40 (C) 60 (D) 140

Answer: (A)

[Click here to watch video explanation](#)

3. Three bells P, Q, and R are rung periodically in a school. P is rung every 20 minutes; Q is rung every 30 minutes and R is rung every 50 minutes.
- If all the three bells are rung at 12:00 PM, when will the three bells ring together again the next time?
- (A) 5:00 PM (B) 5:30 PM (C) 6:00 PM (D) 6:30 PM

Answer: (A)


[Click here to watch video explanation](#)

4. Given below are two statements and four conclusions drawn based on the statements.
- Statement 1: Some bottles are cups.
- Statement 2: All cups are knives.
- Conclusion I: Some bottles are knives.
- Conclusion II: Some knives are cups.
- Conclusion III: All cups are bottles.
- Conclusion IV: All knives are cups.
- Which one of the following options can be logically inferred?
- (A) Only conclusion I and conclusion II are correct
- (B) Only conclusion II and conclusion III are correct
- (C) Only conclusion II and conclusion IV are correct
- (D) Only conclusion III and conclusion IV are correct

Answer: (A)

[Click here to watch video explanation](#)

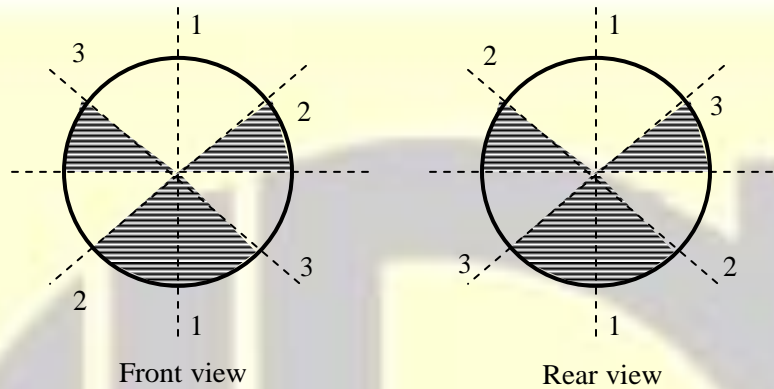5. The figure below shows the front and rear view of a disc, which is shaded with identical patterns. The disc is flipped once with respect to any one of the fixed axes 1-1, 2-2 or 3-3 chosen uniformly at random. What is the probability that the disc DOES NOT retain the same front and rear views after the flipping operation?



- (A) 0 (B) $\frac{1}{3}$ (C) $\frac{2}{3}$ (D) 1

Answer: (C)

[Click here to watch video explanation](#)

Q. No. 6–10 Carry Two Marks Each

6. Altruism is the human concern for the wellbeing of others. Altruism has been shown to be motivated more by social bonding, familiarity and identification of belongingness to a group. The notion that altruism may be attributed to empathy or guilt has now been rejected. Which one of the following is the CORRECT logical inference based on the information in the above passage?
- (A) Humans engage in altruism due to guilt but not empathy
 (B) Humans engage in altruism due to empathy but not guilt
 (C) Humans engage in altruism due to group identification but not empathy
 (D) Humans engage in altruism due to empathy but not familiarity

Answer: (A)

[Click here to watch video explanation](#)

7. There are two identical dice with a single letter on each of the faces. The following six letters: Q, R, S, T, U, and V, one on each of the faces. Any of the six outcomes are equally likely. The two dice are thrown once independently at random. What is the probability that the outcomes on the dice were composed only of any combination of the following possible outcomes: Q, U and V?

(A) $\frac{1}{4}$ (B) $\frac{3}{4}$ (C) $\frac{1}{6}$ (D) $\frac{5}{36}$

Answer: (A)

[Click here to watch video explanation](#)

8. The price of an item is 10% cheaper in an online store S compared to the price at another online store M. Store S charges ₹ 150 for delivery. There are no delivery charges for orders from the store M. A person bought the item from the store S and saved ₹ 100.

What is the price of the item at the online store S (in ₹) if there are no other charges than what is described above?

(A) 2500 (B) 2250 (C) 1750 (D) 1500

Answer: (B)

[Click here to watch video explanation](#)

9. The letters P, Q, R, S, T and U are to be placed one per vertex on a regular convex hexagon, but not necessarily in the same order.

Consider the following statements:

- The line segment joining R and S is longer than the line segment joining P and Q.
- The line segment joining R and S is perpendicular to the line segment joining P and Q.
- The line segment joining R and U is parallel to the line segment joining T and Q.


Based on the above statements, which one of the following options is CORRECT?

- (A) The line segment joining R and T is parallel to the line segment joining Q and S
(B) The line segment joining T and Q is parallel to the line joining P and U
(C) The line segment joining R and P is perpendicular to the line segment joining U and Q
(D) The line segment joining Q and S is perpendicular to the line segment joining R and P

Answer: (A)


[Click here to watch video explanation](#)

10.

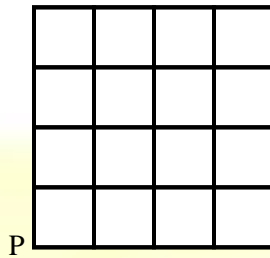

An ant is at the bottom-left corner of a grid (point P) as shown above. It aims to move to the top-right corner of the grid. The ant moves only along the lines marked in the grid such that the current distance to the top-right corner strictly decreases.

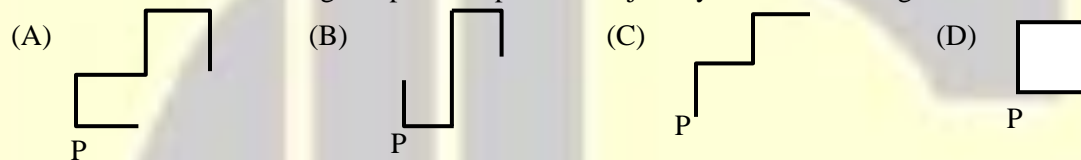Which one of the following is a part of a possible trajectory of the ant during the movement?



Answer: (C)

[Click here to watch video explanation](#)

ELECTRICAL ENGINEERING

Q. No. 11 to 35 Carry One Mark Each

11. The transfer function of a real system, (s), is given as:

$$H(s) = \frac{As + B}{s^2 + Cs + D},$$

where A , B , C and D are positive constants. This system cannot operate as

- (A) low pass filter.
- (B) high pass filter.
- (C) band pass filter.
- (D) an integrator.

Answer: (B or D)

[Click here to watch video explanation](#)

12. For an ideal MOSFET biased in saturation, the magnitude of the small signal current gain for a common drain amplifier is

- (A) 0
- (B) 1
- (C) 100
- (D) infinite

Answer: (D)


[Click here to watch video explanation](#)

13. The most commonly used relay, for the protection of an alternator against loss of excitation, is
- (A) offset Mho relay. (B) over current relay.
(C) differential relay. (D) Buchholz relay.

Answer: (A)

[Click here to watch video explanation](#)

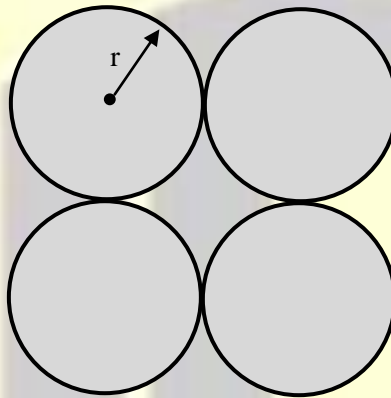14. The geometric mean radius of a conductor, having four equal strands with each strand of radius ' r ', as shown in the figure below, is



- (A) $4r$ (B) $1.414r$ (C) $2r$ (D) $1.723r$

Answer: (D)


[Click here to watch video explanation](#)

15. The valid positive, negative and zero sequence impedances (in p.u.), respectively, for a 220 kV, fully transposed three-phase transmission line, from the given choices are
- (A) 1.1, 0.15 and 0.08 (B) 0.15, 0.15 and 0.35
(C) 0.2, 0.2 and 0.2 (D) 0.1, 0.3 and 0.1

Answer: (B)

[Click here to watch video explanation](#)

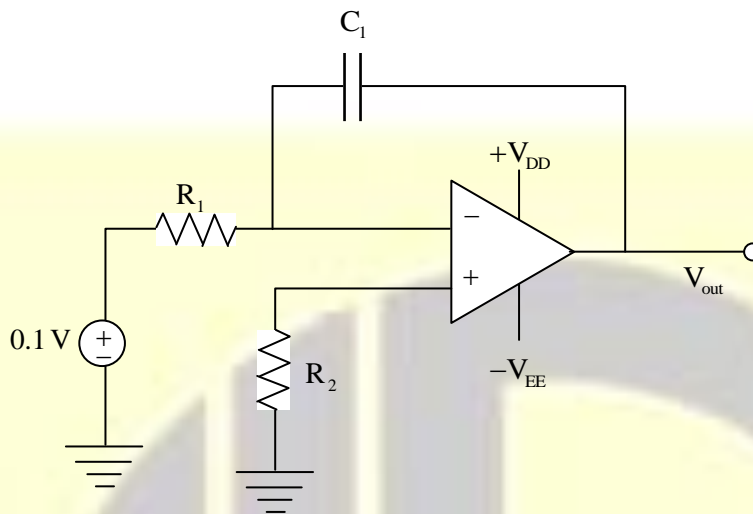16. The steady state output (V_{out}), of the circuit shown below, will




- (A) saturate to $+V_{DD}$
- (B) saturate to $-V_{EE}$
- (C) become equal to 0.1 V
- (D) become equal to -0.1 V

Answer: (B)

[Click here to watch video explanation](#)

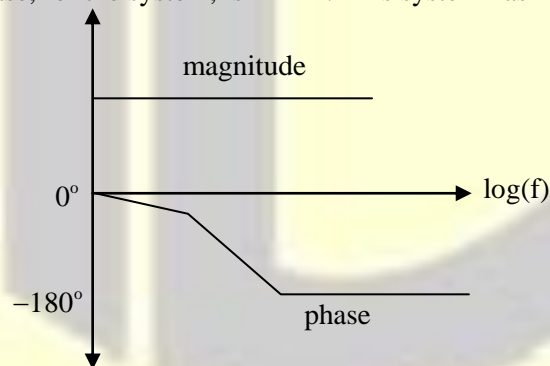17. The Bode magnitude plot of a first order stable system is constant with frequency. The asymptotic value of the high frequency phase, for the system, is -180° . This system has



- (A) one LHP pole and one RHP zero at the same frequency.
- (B) one LHP pole and one LHP zero at the same frequency.
- (C) two LHP poles and one RHP zero.
- (D) two RHP poles and one LHP zero.

Answer: (A)

[Click here to watch video explanation](#)

18. A balanced Wheatstone bridge $ABCD$ has the following arm resistances:

$R_{AB} = 1k\Omega \pm 2.1\%$, $R_{BC} = 100\Omega \pm 0.5\%$; R_{CD} is an unknown resistance;

$R_{DA} = 300\Omega \pm 0.4\%$. The value of R_{CD} and its accuracy is

- (A) $30\Omega \pm 3\Omega$ (B) $30\Omega \pm 0.9\Omega$ (C) $3000\Omega \pm 90\Omega$ (D) $3000\Omega \pm 3\Omega$

Answer: (B)

[Click here to watch video explanation](#)

19. The open loop transfer function of a unity gain negative feedback system is given by $G(s) = \frac{k}{s^2 + 4s - 5}$.

The range of k for which the system is stable, is

- (A) $k > 3$ (B) $k < 3$ (C) $k > 5$ (D) $k < 5$

Answer: (C)

[Click here to watch video explanation](#)


20. Consider a 3×3 matrix A whose (i,j) -th element, $a_{i,j} = (i - j)^3$. Then the matrix A

- (A) symmetric. (B) skew-symmetric. (C) unitary (D) null

Answer: (B)

[Click here to watch video explanation](#)

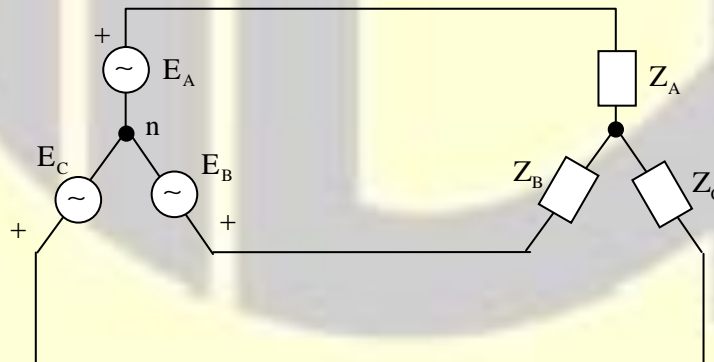21. In the circuit shown below, a three-phase star-connected unbalanced load is connected to a balanced three-phase supply of $100\sqrt{3}V$ with phase sequence ABC . The star connected load has $Z_A = 10\Omega$ and $Z_B = 20\angle 60^\circ\Omega$. The value of Z_C in Ω , for which the voltage difference across the nodes n and n' is zero, is



- (A) $20\angle -30^\circ$ (B) $20\angle 30^\circ$ (C) $20\angle -60^\circ$ (D) $20\angle 60^\circ$

Answer: (C)

[Click here to watch video explanation](#)

22. A charger supplies 100 W at 20 V for charging the battery of a laptop. The power devices, used in the converter inside the charger, operate at a switching frequency of 200 kHz. Which power device is best suited for this purpose?

- (A) IGBT (B) Thyristor
(C) MOSFET (D) BJT

Answer: (C)

[Click here to watch video explanation](#)

23. A long conducting cylinder having a radius 'b' is placed along the z axis. The current density is $J = J_a r^3 \hat{z}$ for the region $r < b$ where r is the distance in the radial direction. The magnetic field intensity (**H**) for the region inside the conductor (i.e. for $r < b$) is

- (A) $\frac{J_a}{4} r^4$ (B) $\frac{J_a}{3} r^3$ (C) $\frac{J_a}{5} r^4$ (D) $J_a r^3$

Answer: (C)

[Click here to watch video explanation](#)


24. The type of single-phase induction motor, expected to have the maximum power factor during steady state running condition, is

- (A) split phase (resistance start). (B) shaded pole.
(C) capacitor start. (D) capacitor start, capacitor run.

Answer: (D)

[Click here to watch video explanation](#)

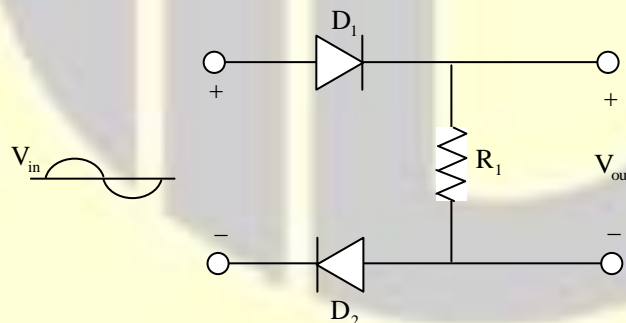25. For the circuit shown below with ideal diodes, the output will be



- (A) $V_{out} = V_{in}$ for $V_{in} > 0$ (B) $V_{out} = V_{in}$ for $V_{in} < 0$
(C) $V_{out} = -V_{in}$ for $V_{in} > 0$ (D) $V_{out} = -V_{in}$ for $V_{in} < 0$

Answer: (A)

[Click here to watch video explanation](#)

26. A MOD 2 and a MOD 5 up-counter when cascaded together results in a MOD _____ counter. (in integer)

Answer: (10 to 10)


[Click here to watch video explanation](#)

27. An inductor having a Q -factor of 60 is connected in series with a capacitor having a Q factor of 240. The overall Q -factor of the circuit is _____. (round off to nearest integer)

Answer: (48 to 48)

[Click here to watch video explanation](#)

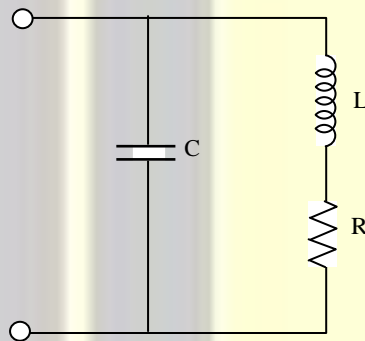28. The network shown below has a resonant frequency of 150 kHz and a bandwidth of 600 Hz. The Q -factor of the network is _____. (round off to nearest integer)



Answer: (250 to 250)

[Click here to watch video explanation](#)

29. The maximum clock frequency in MHz of a 4-stage ripple counter, utilizing flip-flops, with each flip-flop having a propagation delay of 20 ns, is _____. (round off to one decimal place).

Answer: (12.3 to 12.7)


[Click here to watch video explanation](#)

30. If only 5% of the supplied power to a cable reaches the output terminal, the power loss in the cable, in decibels, is _____. (round off to nearest integer)

Answer: (13 to 13)

[Click here to watch video explanation](#)

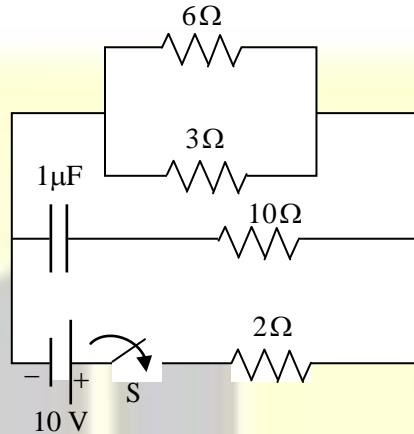31. In the circuit shown below, the switch S is closed at $t = 0$. The magnitude of the steady state voltage, in volts, across the $6\ \Omega$ resistor is _____. (round off to two decimal places).



Answer: (4.95 to 5.05)

[Click here to watch video explanation](#)

32. A single-phase full-bridge diode rectifier feeds a resistive load of $50\ \Omega$ from a $200\ \text{V}$, $50\ \text{Hz}$ single phase AC supply. If the diodes are ideal, then the active power, in watts, drawn by the load is _____. (round off to nearest integer).

Answer: (795 to 805)

[Click here to watch video explanation](#)

33. The voltage at the input of an AC-DC rectifier is given by $v(t) = 230\sqrt{2}\sin\omega t$ where $\omega = 2\pi \times 50\ \text{rad/s}$. The input current drawn by the rectifier is given by


$$i(t) = 10\sin\left(\omega t - \frac{\pi}{3}\right) + 4\sin\left(3\omega t - \frac{\pi}{6}\right) + 3\sin\left(5\omega t - \frac{\pi}{3}\right).$$

The input power factor, (rounded off to two decimal places), is, _____ lag.

Answer: (0.43 to 0.47)

[Click here to watch video explanation](#)

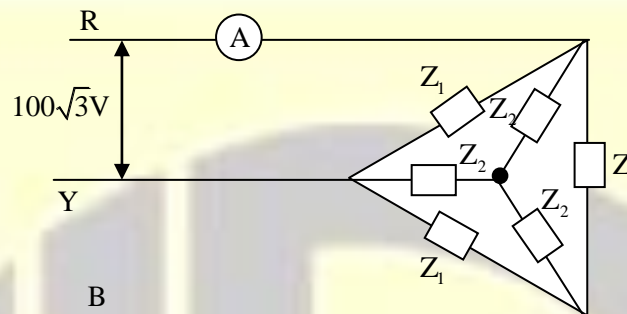34. Two balanced three-phase loads, as shown in the figure, are connected to a $100\sqrt{3}\text{V}$, three-phase, 50 Hz main supply. Given $Z_1 = (18 + j24)\Omega$ and $Z_2 = (6 + j8)\Omega$. The ammeter reading, in amperes, is _____. (round off to nearest integer)



Answer: (20 to 20)

[Click here to watch video explanation](#)

35. The frequencies of the stator and rotor currents flowing in a three-phase 8-pole induction motor are 40 Hz and 1 Hz, respectively. The motor speed, in rpm, is _____. (round off to nearest integer)

Answer: (580 to 590)

[Click here to watch video explanation](#)



GATE REFRESHER COURSE Electrical Engineering






GATEFORUM Pioneers in Digital courses for GATE since 2008 offers **GATE refresher course** giving you access to video solutions for previous 11 years GATE questions and Topic-wise formula Compendium (Handbook).

**Enroll now and get 20% discount use
Promo Code **GATEPAPERS****

For more details visit gateforumonline.com

Q. No. 36–65 Carry Two Marks Each

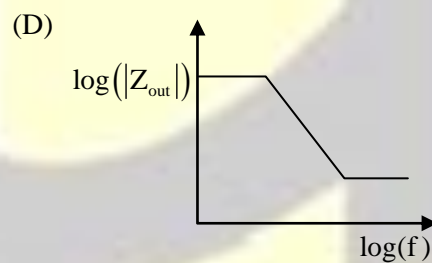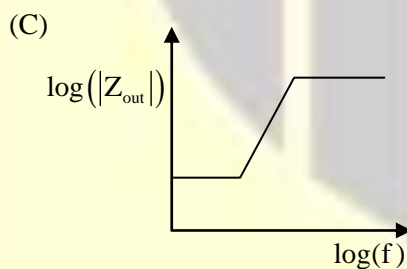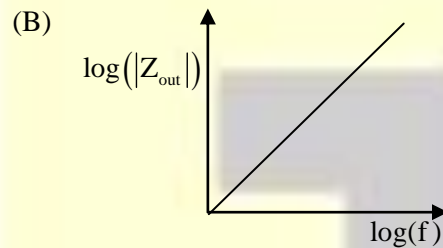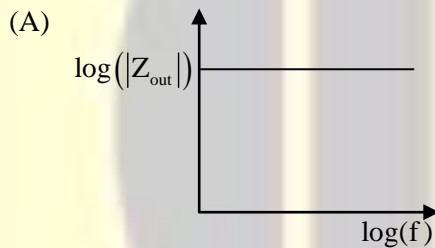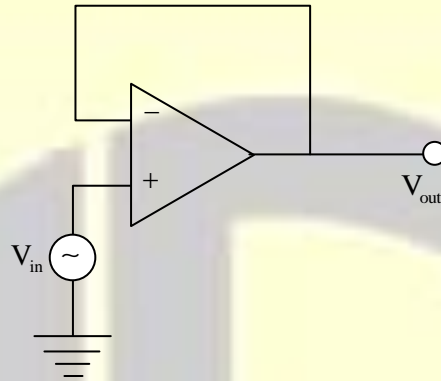36. The output impedance of a non-ideal operational amplifier is denoted by Z_{out} . The variation in the magnitude of Z_{out} with increasing frequency, f , in the circuit shown below, is best represented by



Answer: (C)


[Click here to watch video explanation](#)

37. An LTI system is shown in the figure where

$$G(s) = \frac{100}{s^2 + 0.1s + 10}$$

The steady state output of the system, to the input $r(t)$, is given as

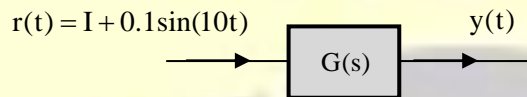$y(t) = a + b \sin(10t + \theta)$. The values of 'a' and 'b' will be



(A) $a = 1, b = 10$

(B) $a = 10, b = 1$

(C) $a = 1, b = 100$

(D) $a = 100, b = 1$


Answer: (A)

[Click here to watch video explanation](#)

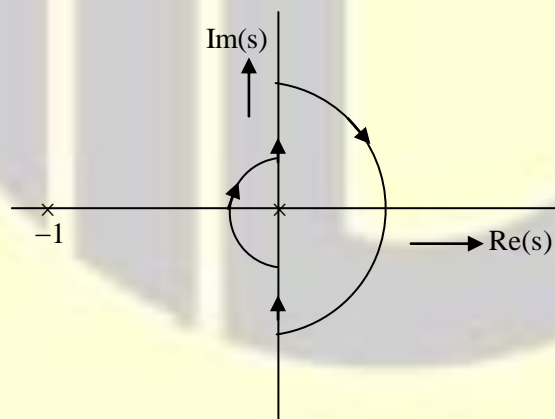38. The open loop transfer function of a unity gain negative feedback system is given as

$$G(s) = \frac{1}{s(s+1)}$$

The Nyquist contour in the s -plane encloses the entire right half plane and a small neighbourhood around the origin in the left half plane, as shown in the figure below. The number of encirclements of the point $(-1 + j0)$ by the Nyquist plot of $G(s)$, corresponding to the Nyquist contour, is denoted as N . Then N equals to



(A) 0

(B) 1


(C) 2

(D) 3

Answer: (B)

[Click here to watch video explanation](#)

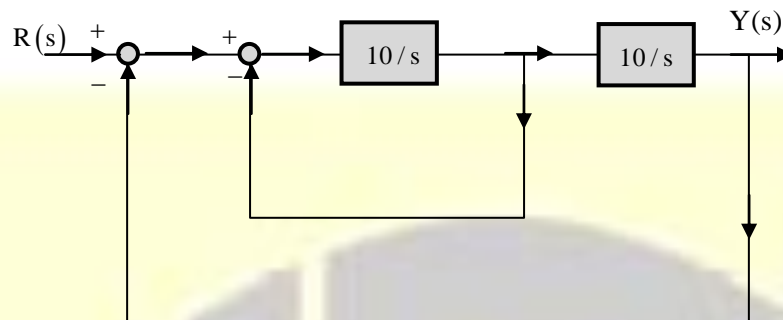39. The damping ratio and undamped natural frequency of a closed loop system as shown in the figure, are denoted as ζ and ω_n , respectively. The values of ζ and ω_n are



- (A) $\zeta = 0.5$ and $\omega_n = 10 \text{ rad/s}$ (B) $\zeta = 0.1$ and $\omega_n = 10 \text{ rad/s}$
 (C) $\zeta = 0.707$ and $\omega_n = 10 \text{ rad/s}$ (D) $\zeta = 0.707$ and $\omega_n = 100 \text{ rad/s}$

Answer: (A)

[Click here to watch video explanation](#)

40. e^A denotes the exponential of a square matrix A. Suppose λ is an eigenvalue and v is the corresponding eigen-vector of matrix A.

Consider the following two statements:

Statement 1: e^λ is an eigenvalue of e^A

Statement 2: v is an eigen-vector of e^A

Which one of the following options is correct?

- (A) Statement 1 is true and statement 2 is false. (B) Statement 1 is false and statement 2 is true.
 (C) Both the statements are correct. (D) Both the statements are false.

Answer: (C)

[Click here to watch video explanation](#)

41. Let $f(x) = \int_0^x e^t(t-1)(t-2) dt$. Then $f(x)$ decreases in the interval

- (A) $x \in (1, 2)$ (B) $x \in (2, 3)$ (C) $x \in (0, 1)$ (D) $x \in (0.5, 1)$

Answer: (A)

[Click here to watch video explanation](#)

42. Consider a matrix $A = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 4 & -2 \\ 0 & 1 & 1 \end{bmatrix}$.

The matrix A satisfies the equation $6A^{-1} = A^2 + cA + dI$, where c and d are scalars and I is the identity matrix.

Then (c + d) is equal to

- (A) 5 (B) 17 (C) -6 (D) 11

Answer: (A)

[Click here to watch video explanation](#)

43. The fuel cost functions in rupees/hour for two 600 MW thermal power plants are given by

Plant 1: $C_1 = 350 + 6P_1 + 0.004P_1^2$

Plant 2: $C_2 = 450 + aP_2 + 0.003P_2^2$


where P_1 and P_2 are power generated by plant 1 and plant 2, respectively, in MW and a is constant. The incremental cost of power (λ) is 8 rupees per MWh. The two thermal power plants together meet a total power demand of 550 MW. The optimal generation of plant 1 and plant 2 in MW, respectively, are

- (A) 200, 350 (B) 250, 300 (C) 325, 225 (D) 350, 200

Answer: (B)

[Click here to watch video explanation](#)

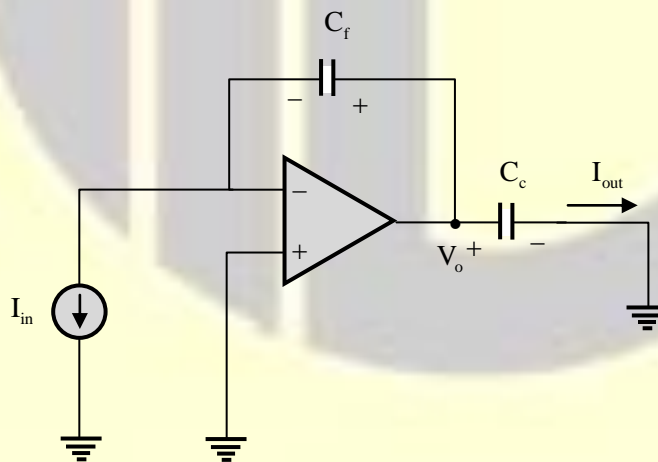44. The current gain (I_{out}/I_{in}) in the circuit with an ideal current amplifier given below is



- (A) $\frac{C_f}{C_c}$ (B) $\frac{-C_f}{C_c}$ (C) $\frac{C_c}{C_f}$ (D) $\frac{-C_c}{C_f}$

Answer: (C)

[Click here to watch video explanation](#)

45. If the magnetic field intensity (H) in a conducting region is given by the expression,

$H = x^2\hat{i} + x^2y^2\hat{j} + x^2y^2z^2\hat{k}$ A / m. The magnitude of the current density, in A/m, at $x = 1$ m, $y = 2$ m, and $z = 1$ m, is

- (A) 8 (B) 12 (C) 16 (D) 20

Answer: (B)

[Click here to watch video explanation](#)

46. Let a causal LTI system be governed by the following differential equation

$y(t) + \frac{1}{4} \frac{dy}{dt} = 2x(t)$, where $x(t)$ and $y(t)$ are the input and output respectively.

Its impulse response is

- (A) $2e^{-\frac{1}{4}t}u(t)$ (B) $2e^{-4t}u(t)$ (C) $8e^{-\frac{1}{4}t}u(t)$ (D) $8e^{-4t}u(t)$

Answer: (D)

[Click here to watch video explanation](#)

47. Let an input $x(t) = 2\sin(10\pi t) + 5\cos(15\pi t) + 7\sin(42\pi t) + 4\cos(45\pi t)$ is passed through an LTI system having an impulse response,

$h(t) = 2\left(\frac{\sin(10\pi t)}{\pi t}\right)\cos(40\pi t)$


The output of the system is

- (A) $2\sin(10\pi t) + 5\cos(15\pi t)$ (B) $5\cos(15\pi t) + 7\sin(42\pi t)$
(C) $7\sin(42\pi t) + 4\cos(45\pi t)$ (D) $2\sin(10\pi t) + 4\cos(45\pi t)$

Answer: (C)

[Click here to watch video explanation](#)

48. Consider the system as shown below

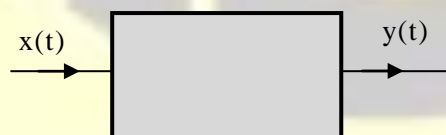

where $y(t) = x(e^t)$. The system is

- (A) linear and causal. (B) linear and non-causal.
(C) non-linear and causal. (D) non-linear and non-causal

Answer: (B)

[Click here to watch video explanation](#)

49. The discrete time Fourier series representation of a signal $x[n]$ with period N is written as $x[n] = \sum_{k=0}^{N-1} a_k e^{j(2k\pi n/N)}$. A discrete time periodic signal with period $N = 3$, has the non-zero Fourier series coefficient: $a_{-3} = 2$ and $a_4 = 1$. The signal is

- (A) $2 + 2e^{-j\left(\frac{2\pi}{6}n\right)} \cos\left(\frac{2\pi}{6}n\right)$ (B) $1 + 2e^{j\left(\frac{2\pi}{6}n\right)} \cos\left(\frac{2\pi}{6}n\right)$
 (C) $1 + 2e^{j\left(\frac{2\pi}{3}n\right)} \cos\left(\frac{2\pi}{6}n\right)$ (D) $2 + 2e^{j\left(\frac{2\pi}{6}n\right)} \cos\left(\frac{2\pi}{6}n\right)$

Answer: (B)

[Click here to watch video explanation](#)


50. Let, $f(x, y, z) = 4x^2 + 7xy + 3xz^2$. The direction in which the function $f(x, y, z)$ increases most rapidly at point $P = (1, 0, 2)$ is

- (A) $20\hat{i} + 7\hat{j}$ (B) $20\hat{i} + 7\hat{j} + 12\hat{k}$ (C) $20\hat{i} + 12\hat{k}$ (D) $20\hat{i}$

Answer: (B)

[Click here to watch video explanation](#)

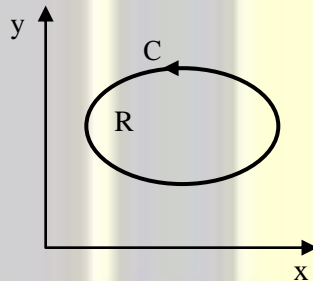51. Let R be a region in the first quadrant of the xy plane enclosed by a closed curve C considered in counter-clockwise direction. Which of the following expressions does not represent the area of the region R ?



- (A) $\iint_R dx dy$ (B) $\oint_C x dy$ (C) $\oint_C y dx$ (D) $\frac{1}{2} \oint_C (x dy - y dx)$

Answer: (C)

[Click here to watch video explanation](#)


52. Let $\vec{E}(x, y, z) = 2x^2\hat{i} + 5y\hat{j} + 3z\hat{k}$. The value of $\iiint_V (\vec{\nabla} \cdot \vec{E}) dV$, where V is the volume enclosed by the unit cube defined by $0 \leq x \leq 1, 0 \leq y \leq 1$, and $0 \leq z \leq 1$, is

- (A) 3 (B) 8 (C) 10 (D) 5

Answer: (C)

[Click here to watch video explanation](#)

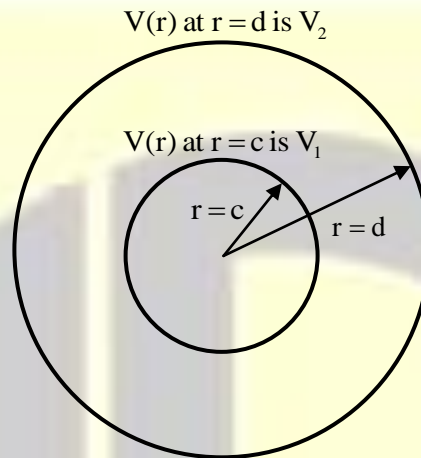53. As shown in the figure below, two concentric conducting spherical shells, centered at $r = 0$ and having radii $r = c$ and $r = d$ are maintained at potentials such that the potential $V(r)$ at $r = c$ is V_1 and $V(r)$ at $r = d$ is V_2 . Assume that $V(r)$ depends only on r , where r is the radial distance. The expression for $V(r)$ in the region between $r = c$ and $r = d$ is



- (A) $V(r) = \frac{cd(V_2 - V_1)}{(d-c)r} - \frac{V_1c + V_2d - 2V_1d}{d-c}$
- (B) $V(r) = \frac{cd(V_1 - V_2)}{(d-c)r} + \frac{V_2d - V_1c}{d-c}$
- (C) $V(r) = \frac{cd(V_1 - V_2)}{(d-c)r} - \frac{V_1c - V_2c}{d-c}$
- (D) $V(r) = \frac{cd(V_2 - V_1)}{(d-c)r} - \frac{V_2c - V_1c}{d-c}$

Answer: (B)

[Click here to watch video explanation](#)

54. Let the probability density function of a random variable x be given as


$$f(x) = ae^{-2|x|}$$

The value of 'a' is _____ .

Answer: (0.99 to 1.01)

[Click here to watch video explanation](#)

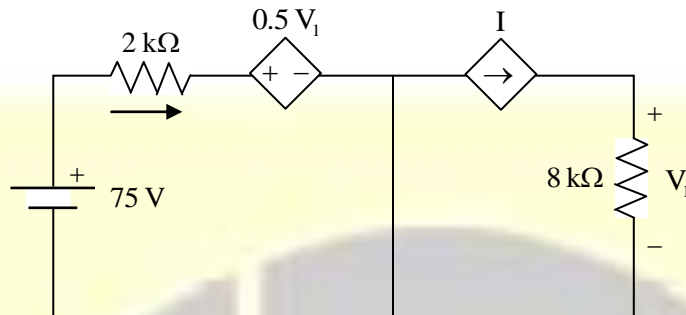55. In the circuit shown below, the magnitude of the voltage V in volts, across the $8k\Omega$ resistor is _____. (round off to nearest integer)



Answer: (98 to 1.01)

[Click here to watch video explanation](#)

56. Two generating units rated for 250 MW and 400 MW have governor speed regulations of 6% and 6.4%, respectively, from no load to full load. Both the generating units are operating in parallel to share a load of 500 MW. Assuming free governor action, the load shared in MW, by the 250 MW generating unit is _____. (round off to nearest integer)

Answer: (188 to 192 or 198 to 202)


[Click here to watch video explanation](#)

57. A 20 MVA, 11.2 kV, 4-pole, 50 Hz alternator has an inertia constant of 15 MJ/MVA. If the input and output powers of the alternator are 15 MW and 10 MW, respectively, the angular acceleration in mechanical degree/ s^2 _____. (round off to nearest integer)

Answer: (74 to 76)

[Click here to watch video explanation](#)

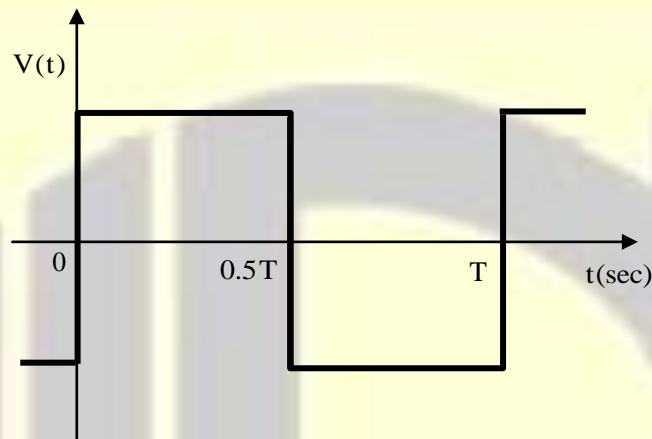58. Consider an ideal full-bridge single-phase DC-AC inverter with a DC bus voltage magnitude of 1000 V. The inverter output voltage $v(t)$ shown below, is obtained when diagonal switches of the inverter are switched with 50 % duty cycle. The inverter feeds a load with a sinusoidal current given by, $i(t) = 10\sin\left(\omega t - \frac{\pi}{3}\right)$ A, where $\omega = \frac{2\pi}{T}$.




The active power, in watts, delivered to the load is _____.(round off to nearest integer)

Answer: (3170 to 3190)

[Click here to watch video explanation](#)

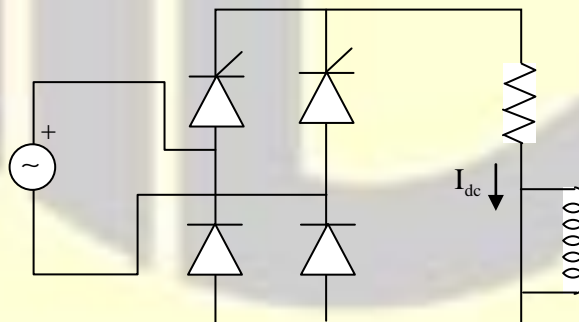59. For the ideal AC-DC rectifier circuit shown in the figure below, the load current magnitude is $I_{dc} = 15$ A and is ripple free. The thyristors are fired with a delay angle of 45° . The amplitude of the fundamental component of the source current, in amperes, is _____. (round off to two decimal places)



Answer: (17.3 to 18)


[Click here to watch video explanation](#)

60. A 3-phase grid-connected voltage source converter with DC link voltage of 1000 V is switched using sinusoidal Pulse Width Modulation (PWM) technique. If the grid phase current is 10 A and the 3-phase complex power supplied by the converter is given by $(-4000 - j3000)$ VA, then the modulation index used in sinusoidal PWM is _____. (round off to two decimal places)

Answer: (0.46 to 0.48)

[Click here to watch video explanation](#)

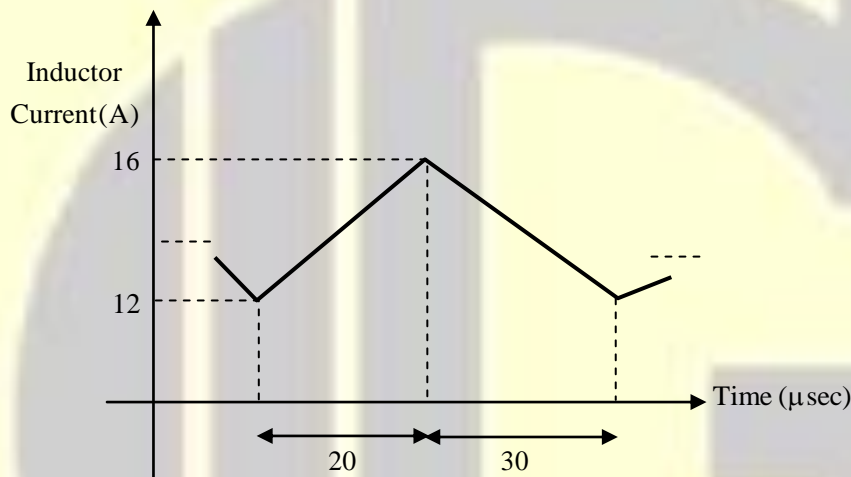61. The steady state current flowing through the inductor of a DC-DC buck boost converter is given in the figure below. If the peak-to-peak ripple in the output voltage of the converter is 1V, then the value of the output capacitor, in μF , is _____. (round off to decimal integer)



Answer: (165 to 171)


[Click here to watch video explanation](#)

62. A 280 V, separately excited DC motor with armature resistance of $1\ \Omega$ and constant field excitation drives a load. The load torque is proportional to the speed. The motor draws a current of 30 A when running at a speed of 1000 rpm. Neglect frictional losses in the motor. The speed, in rpm, at which the motor will run, if an additional resistance of value $10\ \Omega$ is connected in series with the armature, is _____. (round off to nearest integer)

Answer: (480 to 485)

[Click here to watch video explanation](#)

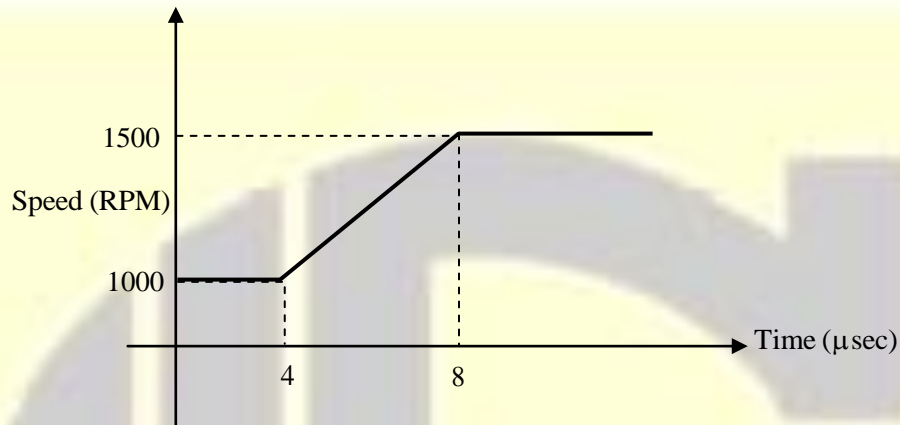63. A 4-pole induction motor with inertia of 0.1 kg-m^2 drives a constant load torque of 2 Nm . The speed of the motor is increased linearly from 1000 rpm to 1500 rpm in 4 seconds as shown in the figure below. Neglect losses in the motor. The energy, in joules, consumed by the motor during the speed change is _____. (round off to nearest integer)



Answer: (675 to 700 or 1725 to 1740)

[Click here to watch video explanation](#)

64. A star-connected 3-phase, 400 V , 50 kVA , 50 Hz synchronous motor has a synchronous reactance of 1 ohm per phase with negligible armature resistance. The shaft load on the motor is 10 kW while the power factor is 0.8 leading. The loss in the motor is 2 kW . The magnitude of the per phase excitation emf of the motor, in volts, is _____. (round off to nearest integer).

Answer: (240 to 248)

[Click here to watch video explanation](#)

65. A 3-phase, 415 V , 4-pole, 50 Hz induction motor draws 5 times the rated current at rated voltage at starting. It is required to bring down the starting current from the supply to 2 times of the rated current using a 3-phase autotransformer. If the magnetizing impedance of the induction motor and no load current of the autotransformer is neglected, then the transformation ratio of the autotransformer is given by _____. (round off to two decimal places).

Answer: (0.61 to 0.65)

[Click here to watch video explanation](#)





Follow us @



For more details visit gateforumonline.com